

# A/C Generator Systems

# What is the function of the charging system?

Provide power for all electrical loads

Recharge the starting battery

What happens if the charging systems puts out too much power?

↑ Voltage goes UP ↑

What happens if the charging system puts out too little power?

↓ Voltage goes DOWN ↓

What is the proper system voltage?

13.8 - 14.8 volts

27.4 – 28.4 volts

What controls the system voltage?

Voltage regulator

How many volts in a fully  
charged battery?

12.6 volts

25.2 volts

After removing surface charge

# How do you check for an Over-charging alternator?

Insure battery is fully charged

Run the engine

Turn Off electrical loads

System voltage below...

...14.8 Volts or 28.4 volts

When less than 8 amps enter  
battery

# What can cause the charging system to Over-charge?

Defective Voltage Regulator

Volt Drop in Voltage Sensing Wire

Volt Drop in regulator ground

Having regulator inside generator eliminates volt drop as a cause for Over-Charging



# How do you check for an Under-charging alternator?

Insure battery is fully charged

Run ALL electrical loads

Run engine at 1,500 RPM

System voltage above...

...13.8 Volts or 27.4 volts

# How else do you check for an undercharging alternator?

Run engine at 1,500 RPM

Load battery with carbon pile to 13 volts (26 volts)

Measure amps leaving generator

Should be at least 90% of rated capacity

# What can cause the charging system to under-charge?

Loose fan belt

Low engine RPM

Excessive load requirements  
(add on accessories)

What can cause the charging system to under-charge?

Short driving trips

Defective generator

Defective voltage regulator

Defective wiring

# Understand the A/C Generator (Alternator)

Identify the following components

Rotor

Stator

Slip rings

Brushes

Diodes or Rectifier

Rotor, creates spinning magnetic field





Stator, creates alternating current





Slip Rings, allow field current into the rotor





Brushes, allow field current into rotor

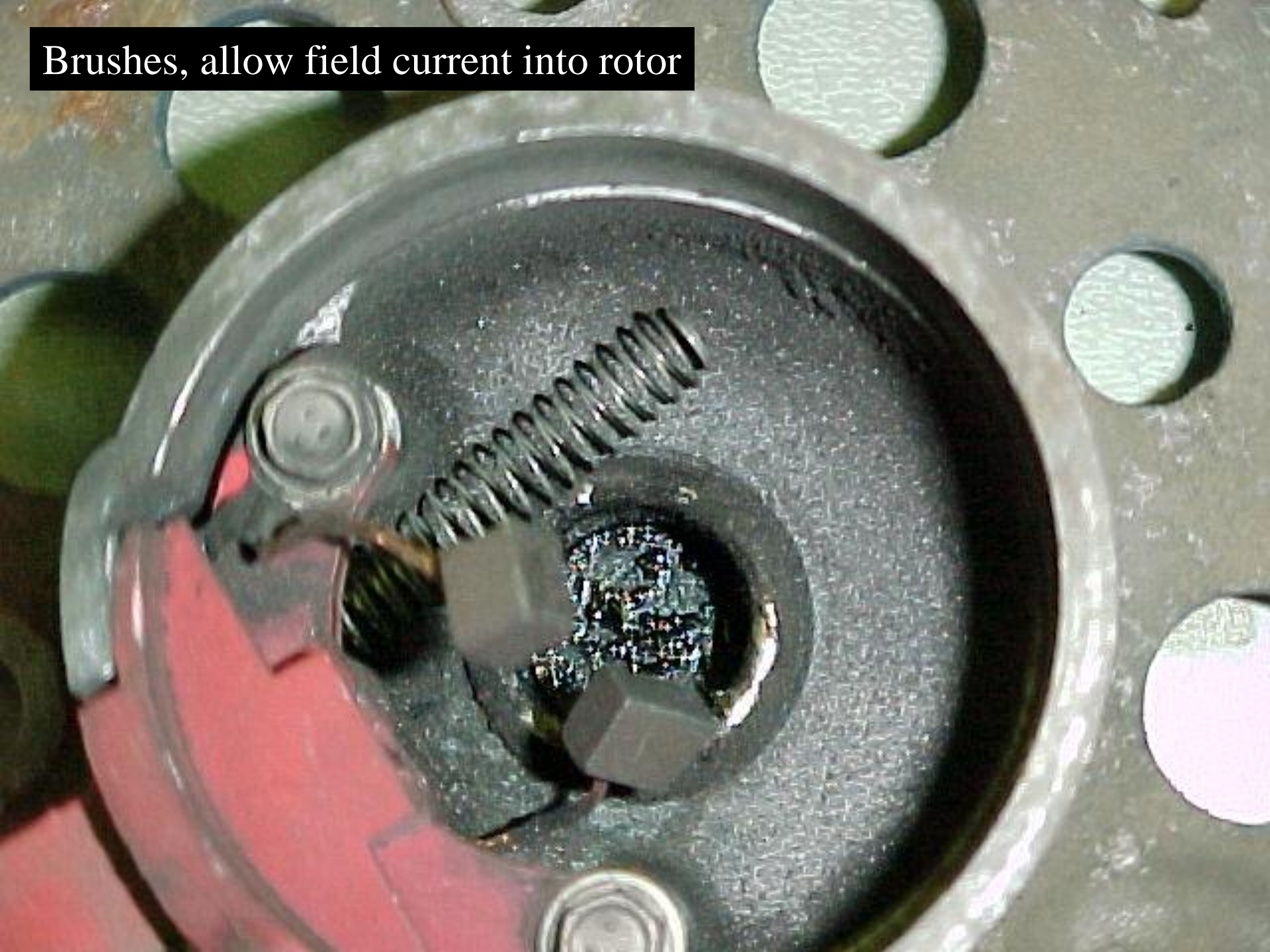

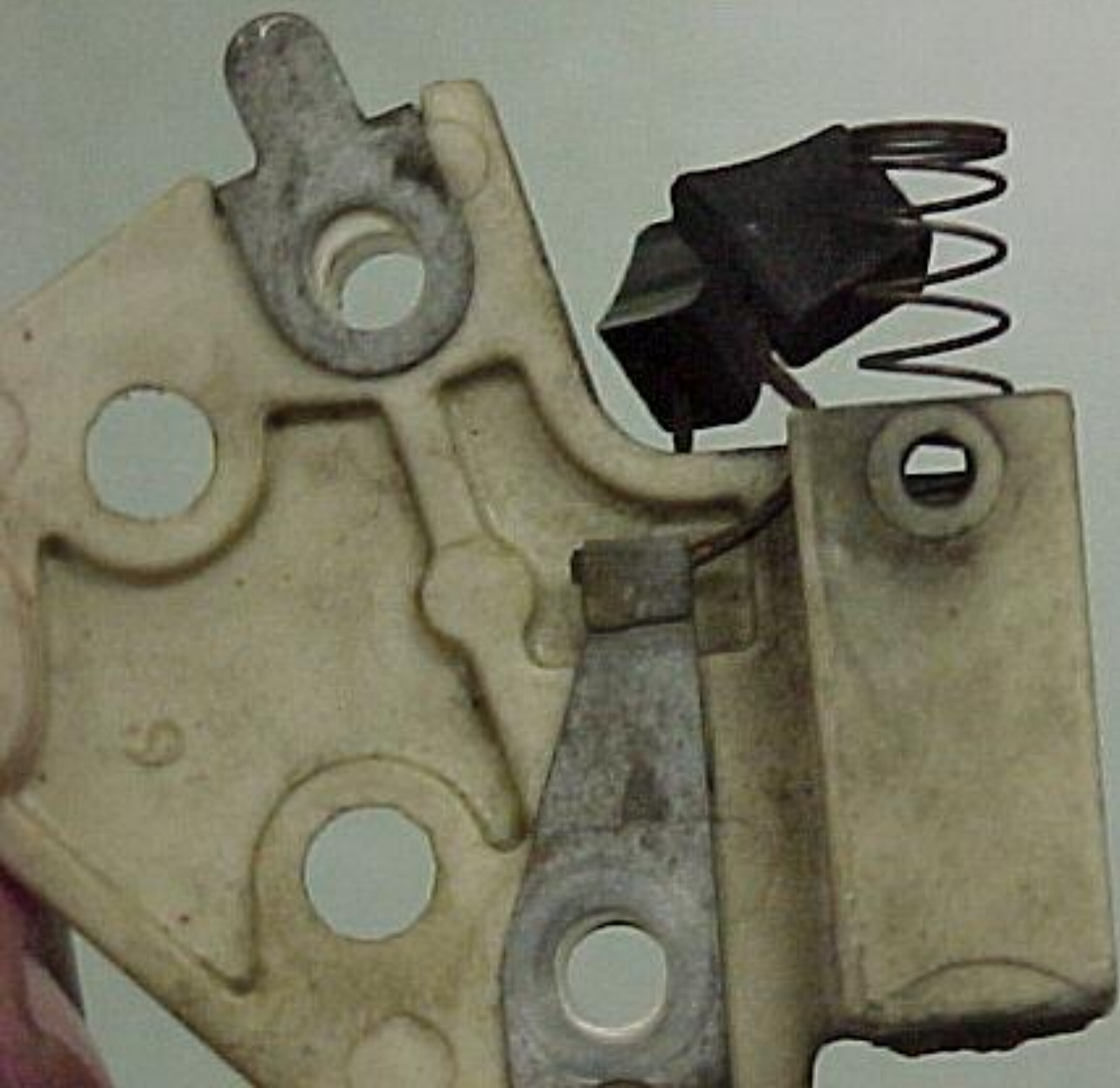




High tech brush installation tool





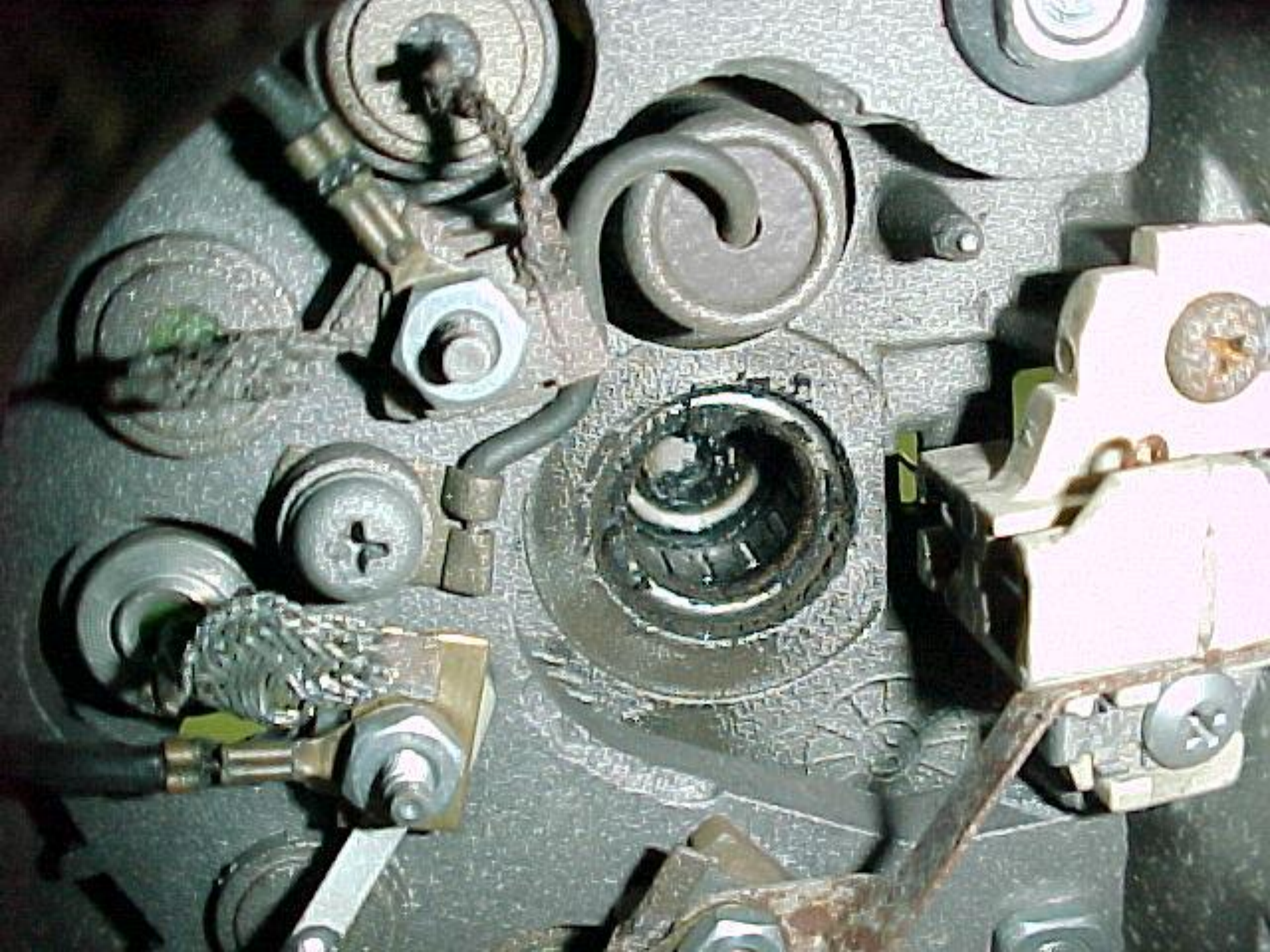






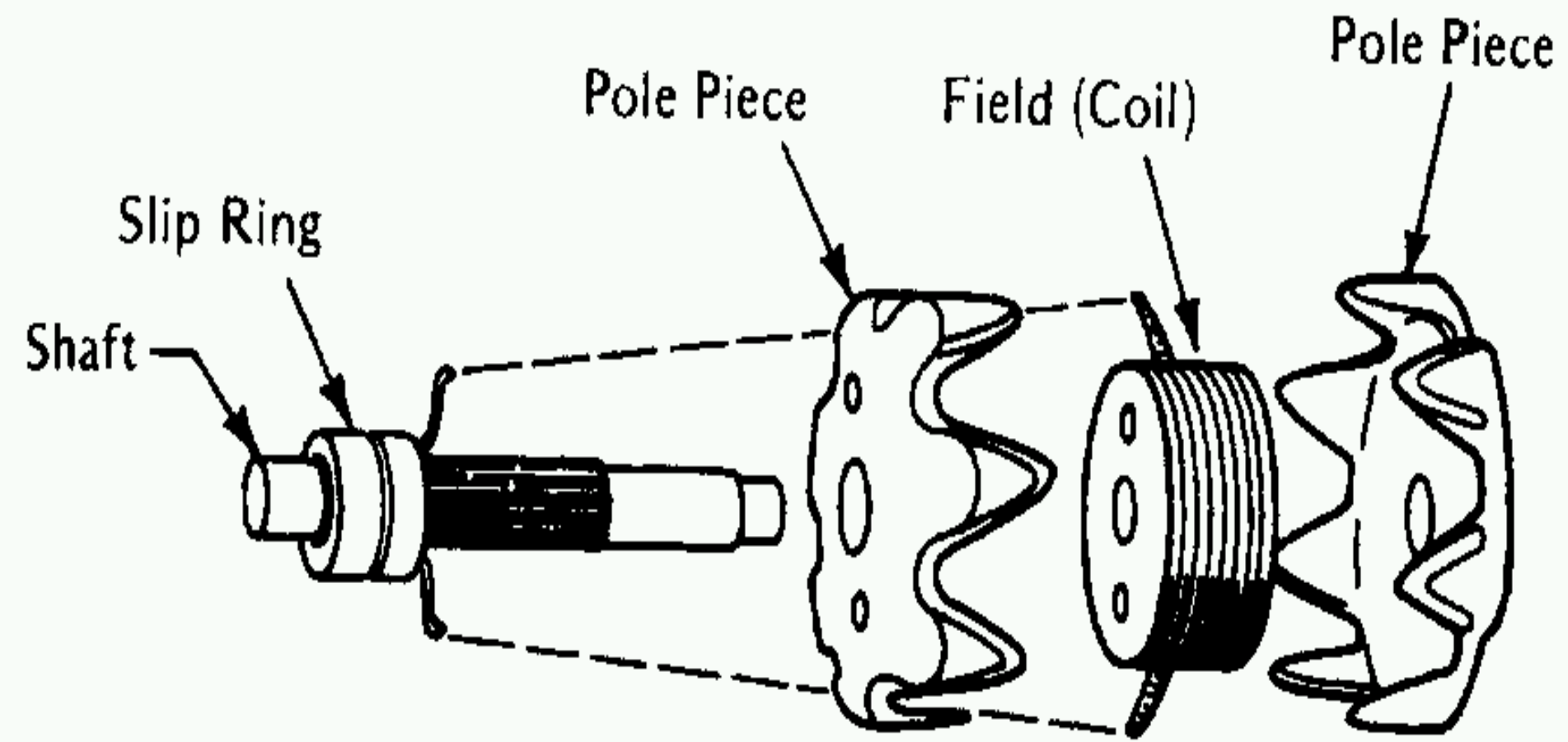
# Rotor (Field)

What does the Rotor do?

Creates a spinning magnetic field inside the A/C generator



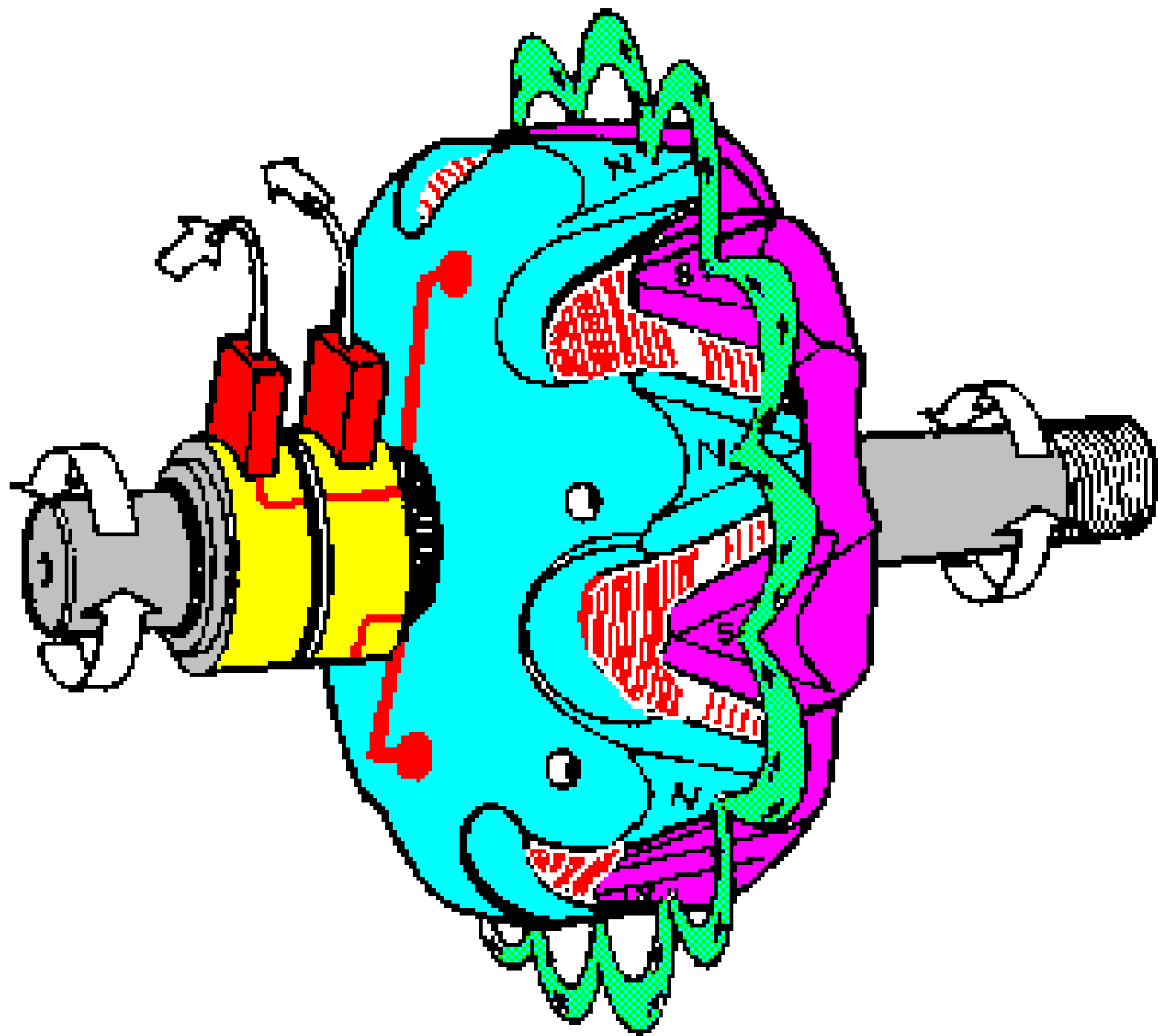



# How do you test the rotor?

Slip rings must be clean and smooth

Field windings must not be open circuit

Field windings must not be shorted  
to ground




Clean slip rings

This image shows a side-by-side comparison of two slip rings. The top slip ring is clean, with a smooth, polished brass surface. The bottom slip ring is burned, with a dark, charred, and uneven surface. Both slip rings are mounted on a metal shaft. The background is a plain, light-colored surface.

Burned slip rings

$\Omega$  L  $\Omega$


Good Rotor

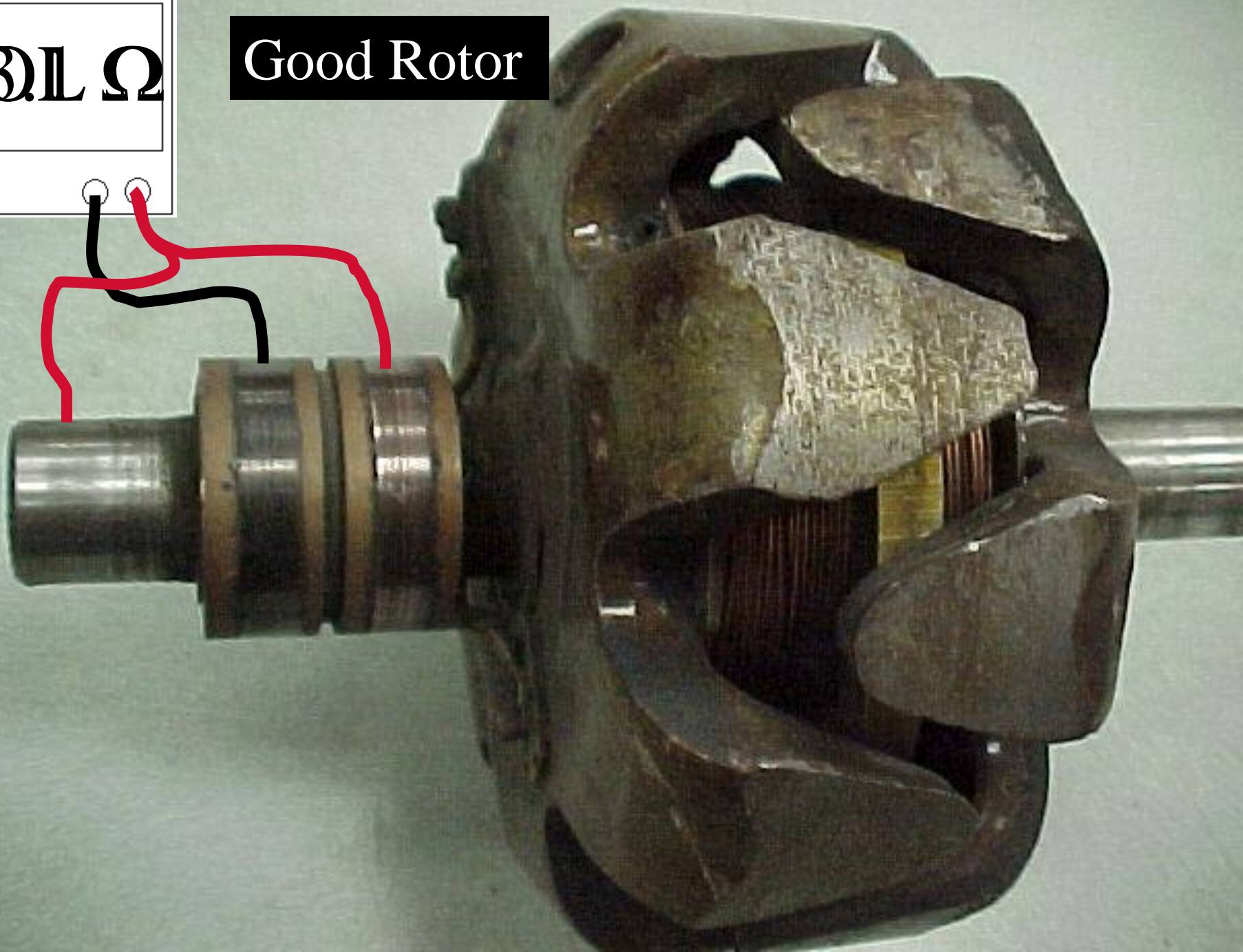



$\Omega$   $\mathbb{E}$   $\Omega$

Bad Rotor

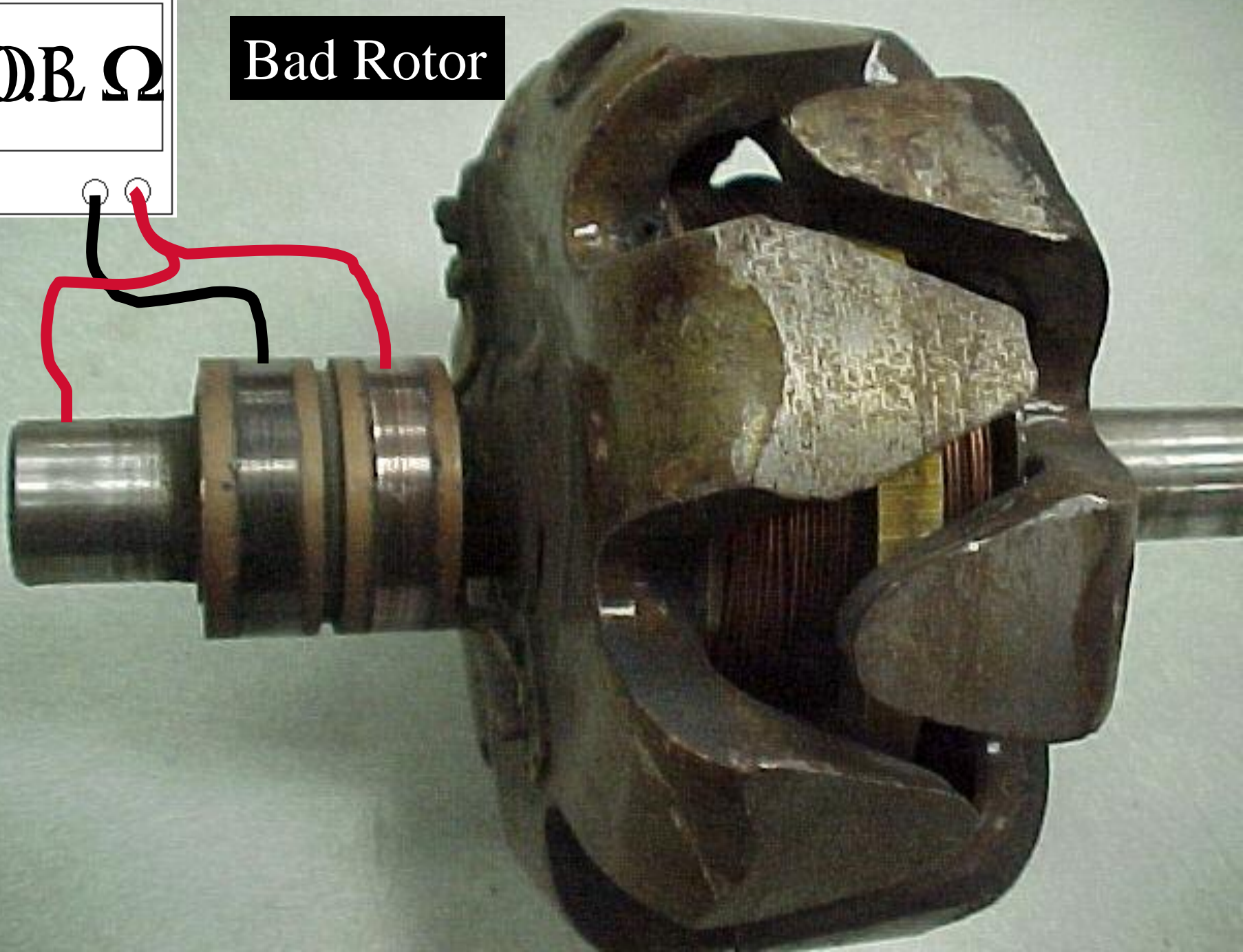

# Stator Windings


What does the Stator do?

Creates electrical power when a magnetic field is moved past it

Creates power to recharge battery and run electrical loads

What does the Stator do?

Creates an Alternating Current

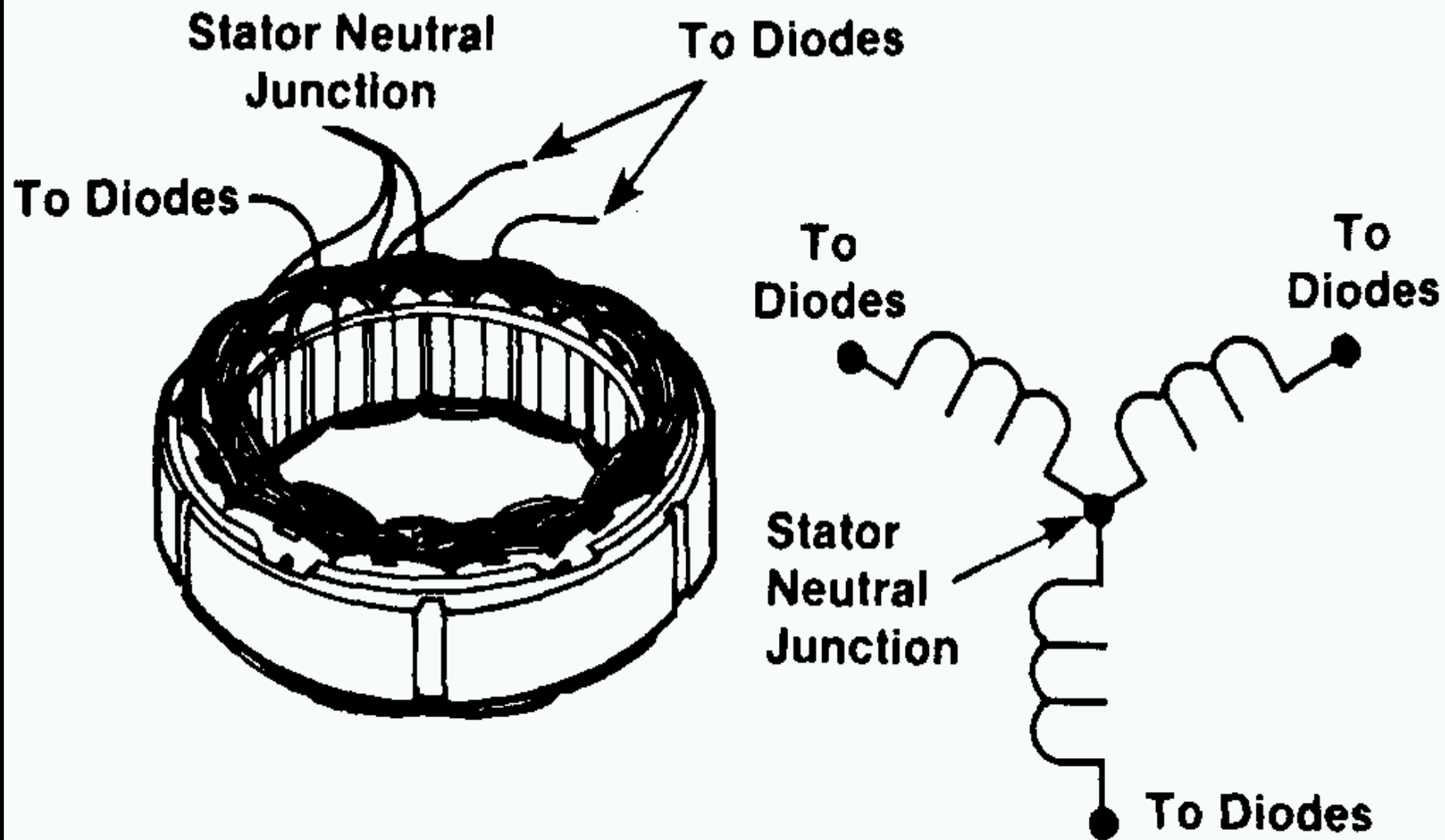

**WYE CONNECTION**


**To Diodes**

**To  
Diodes**

**To Diodes**


**To Diodes**

**DELTA CONNECTION**

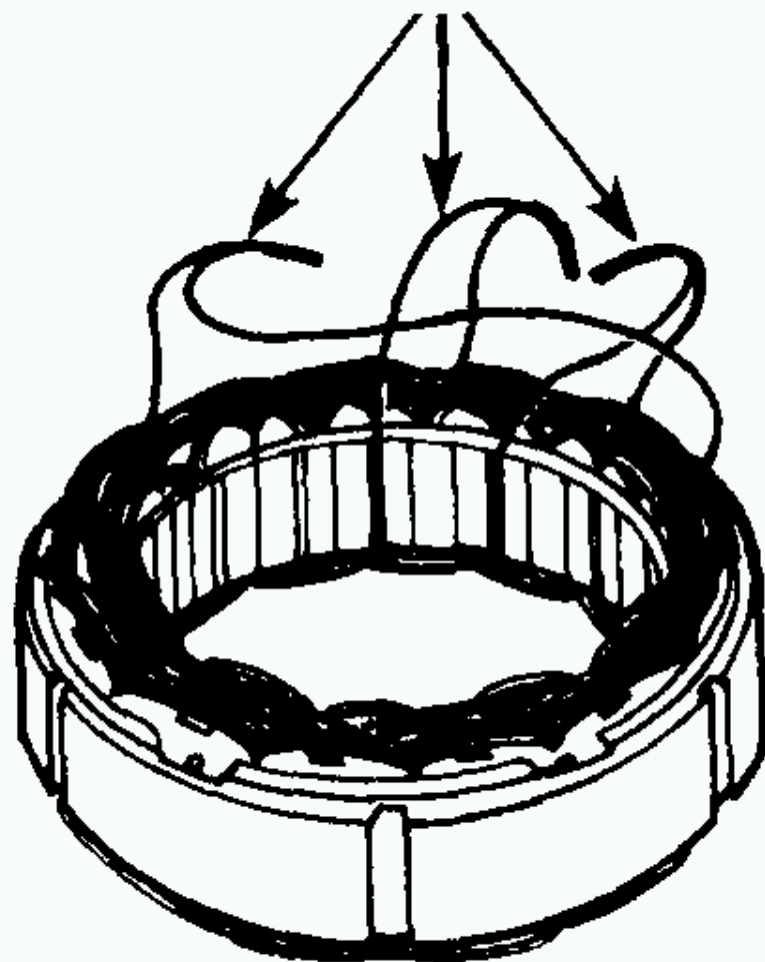




## Voltage Trace for One Stator Winding

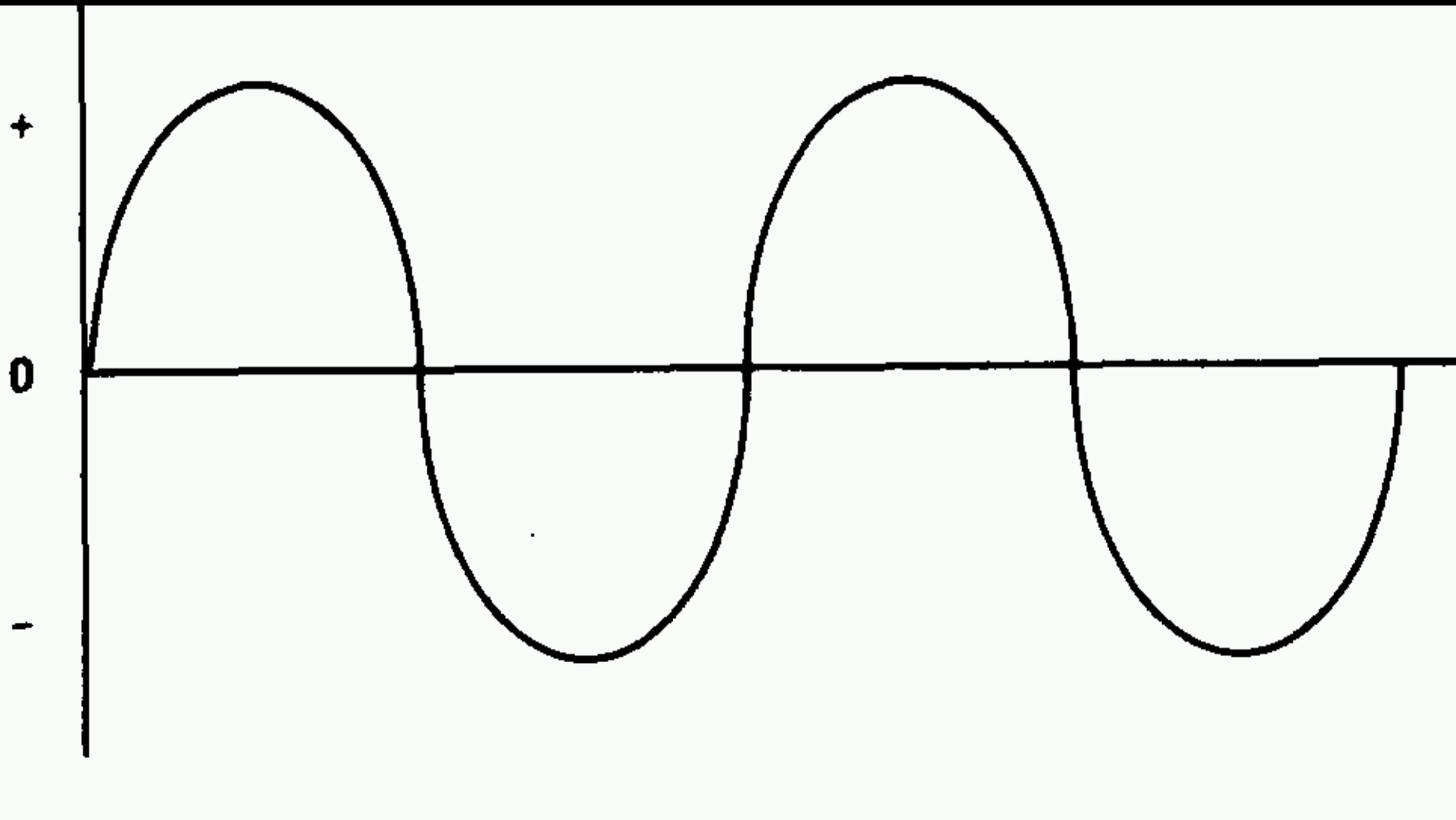
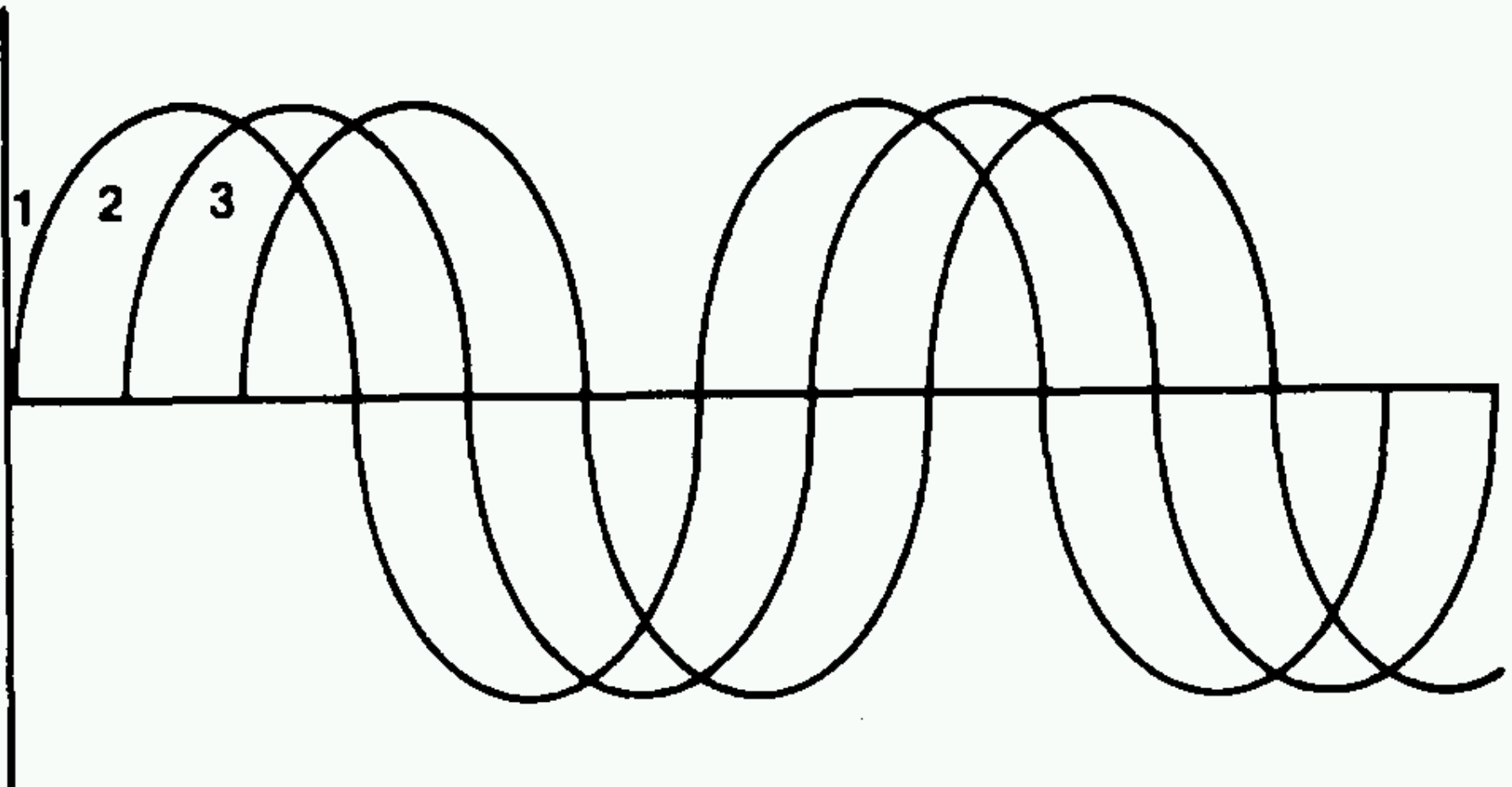
# Voltage Trace for Three Stator Windings




# How do you test the Stator?

Test for open circuits in the windings

Test for grounded windings



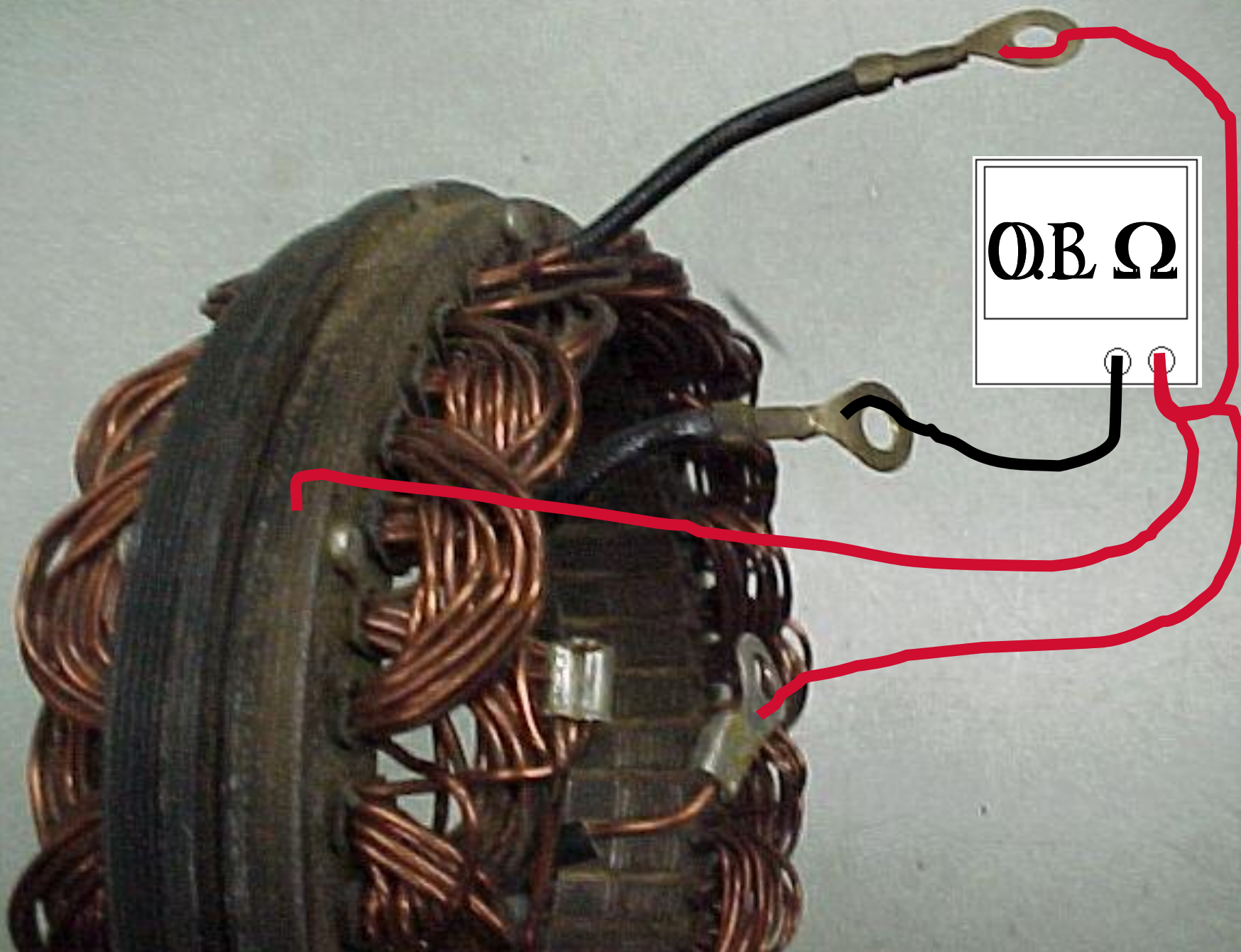
Visually inspect for burning or  
overheated windings



# How does the A/C current change into D/C current

Diodes are used for  
Full Wave Rectification



Diodes are often called rectifiers

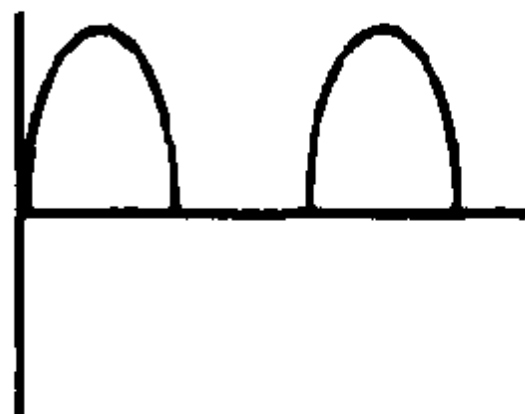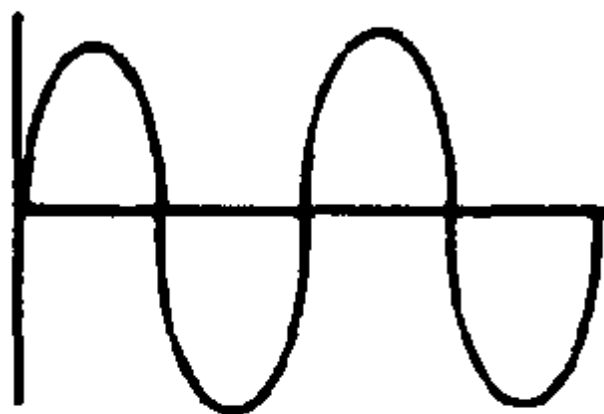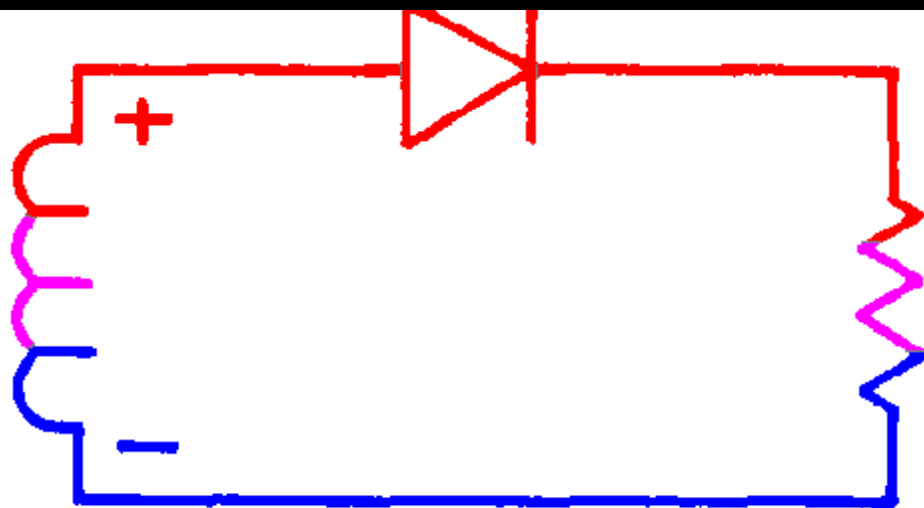

**Half Wave Rectification**

**Diode is positive biased**


**Current is flowing**

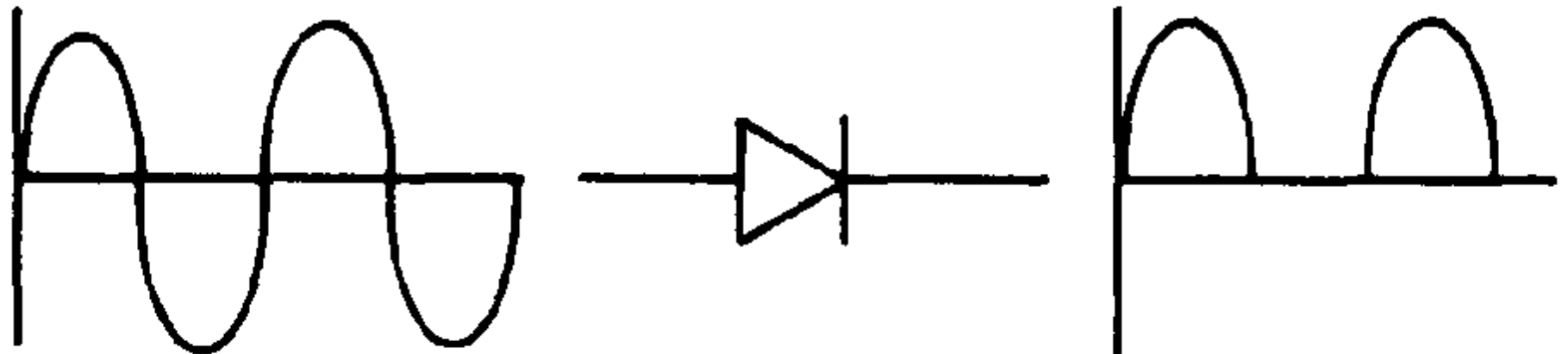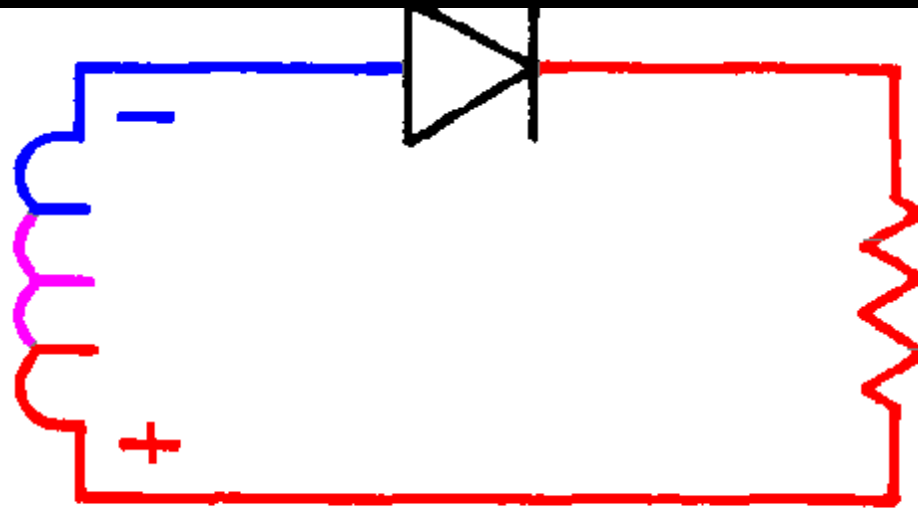

**Half Wave Rectification**


**Diode is reverse biased**

**Current is blocked**

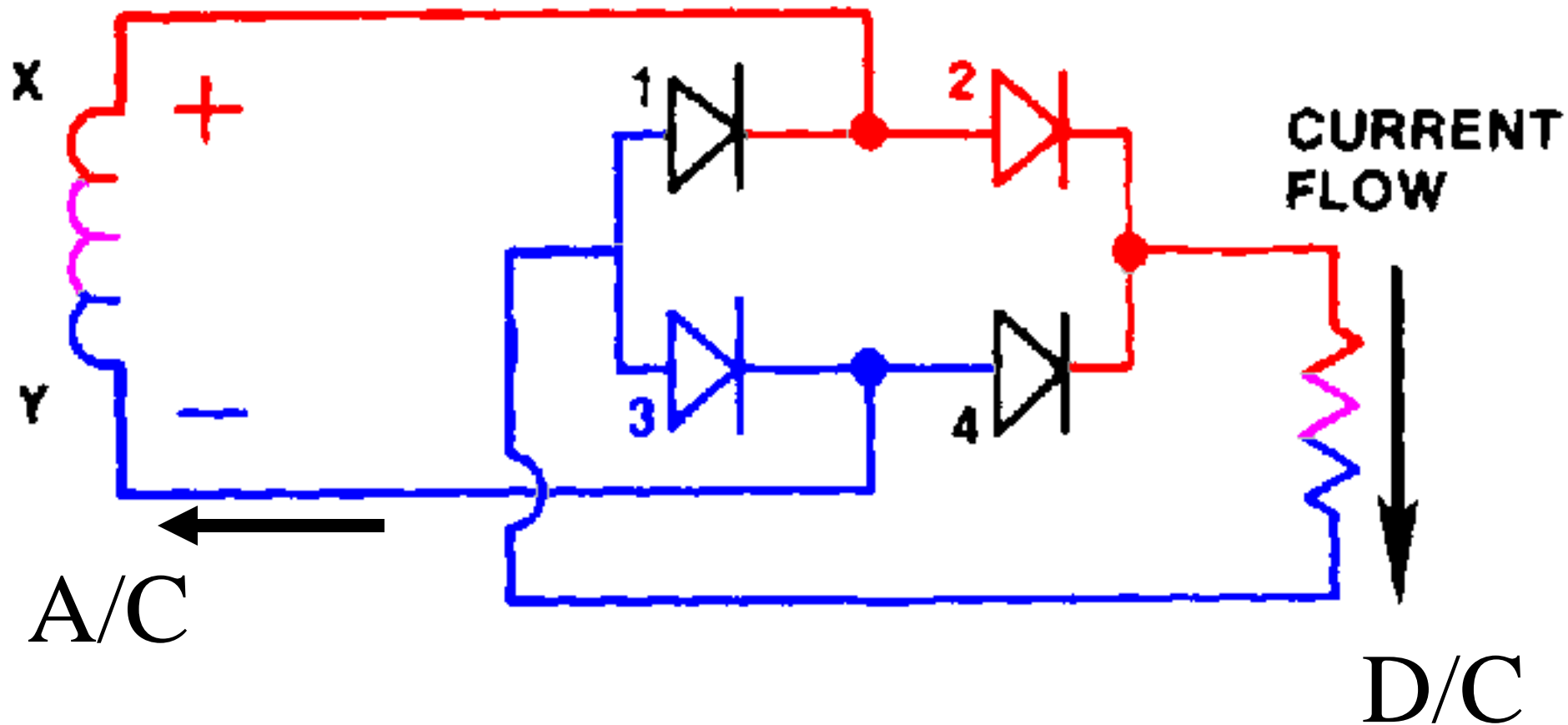


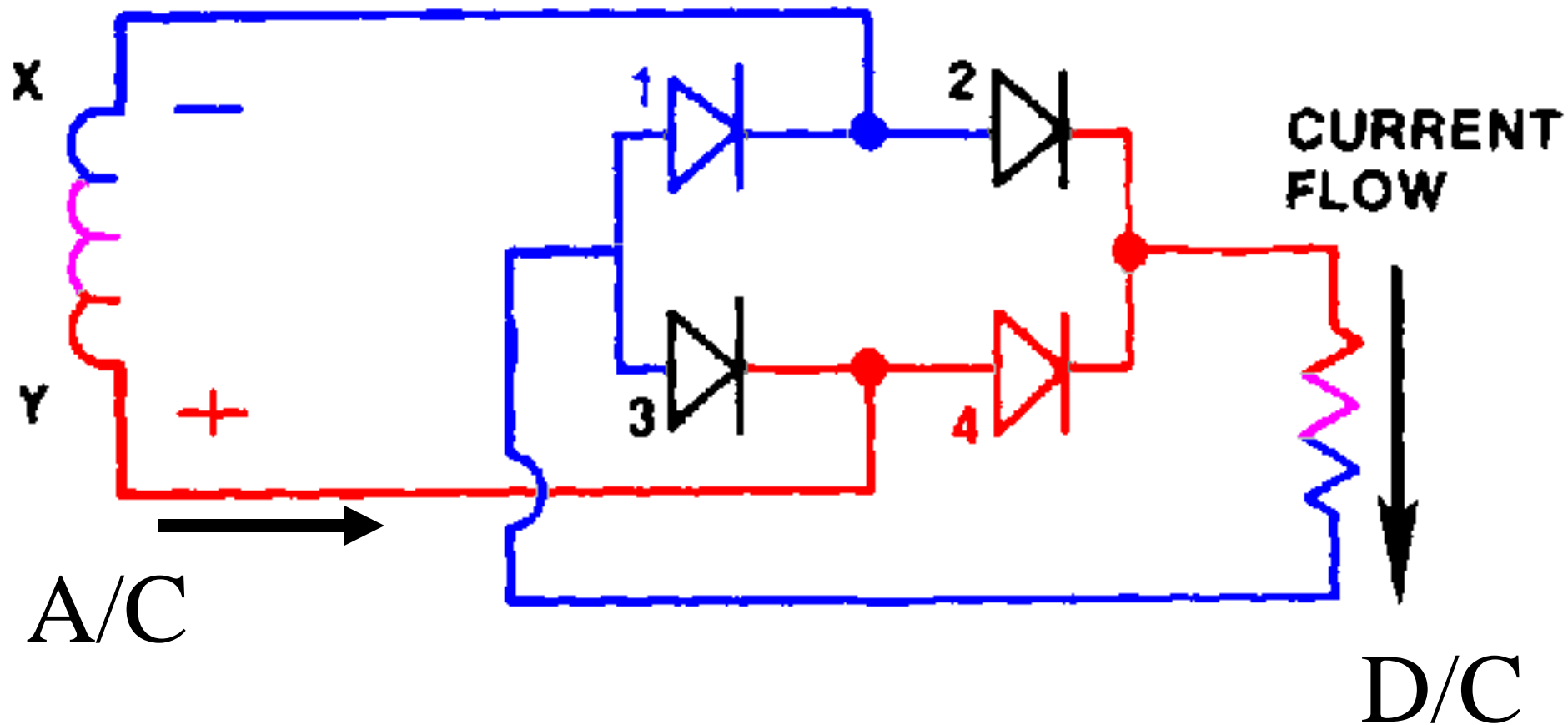Full Wave Rectification ...  
... one stator winding






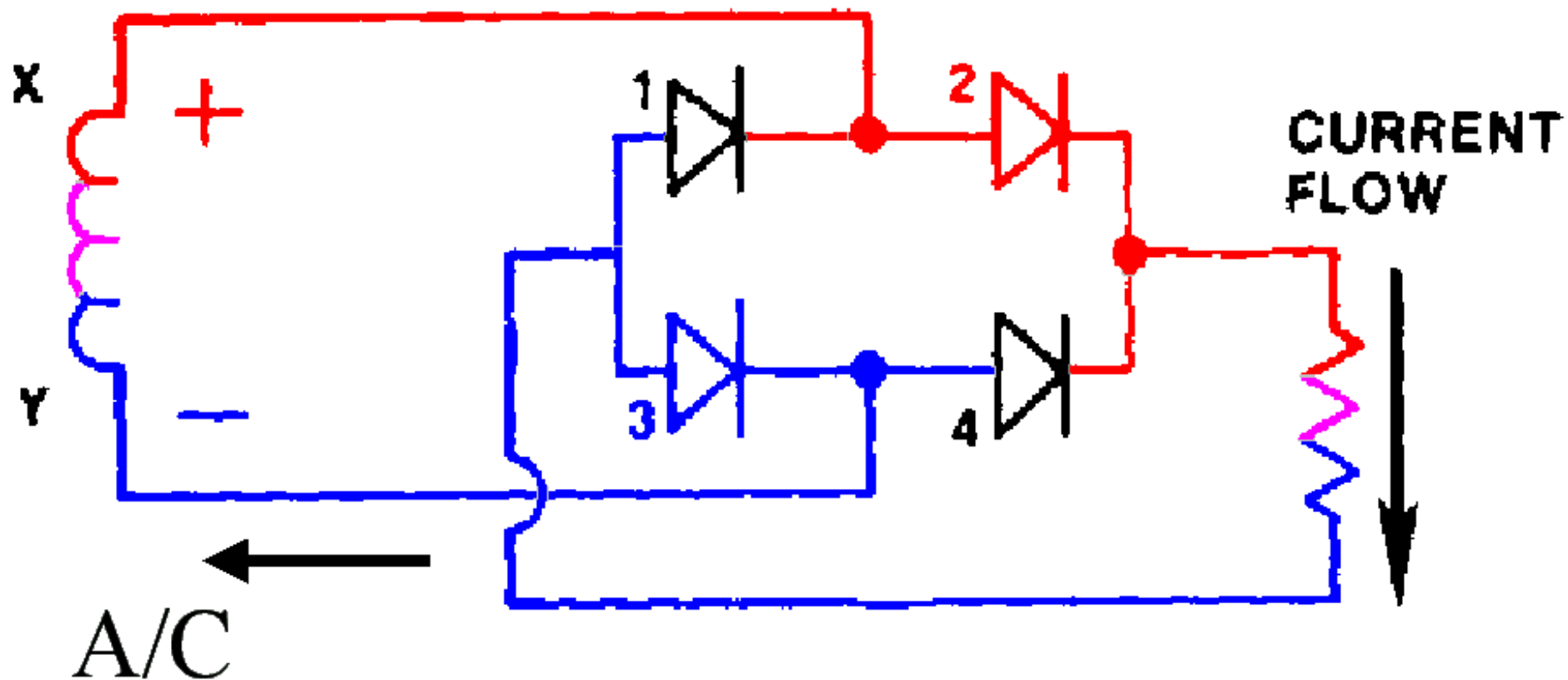
Full Wave Rectification ...  
... one stator winding



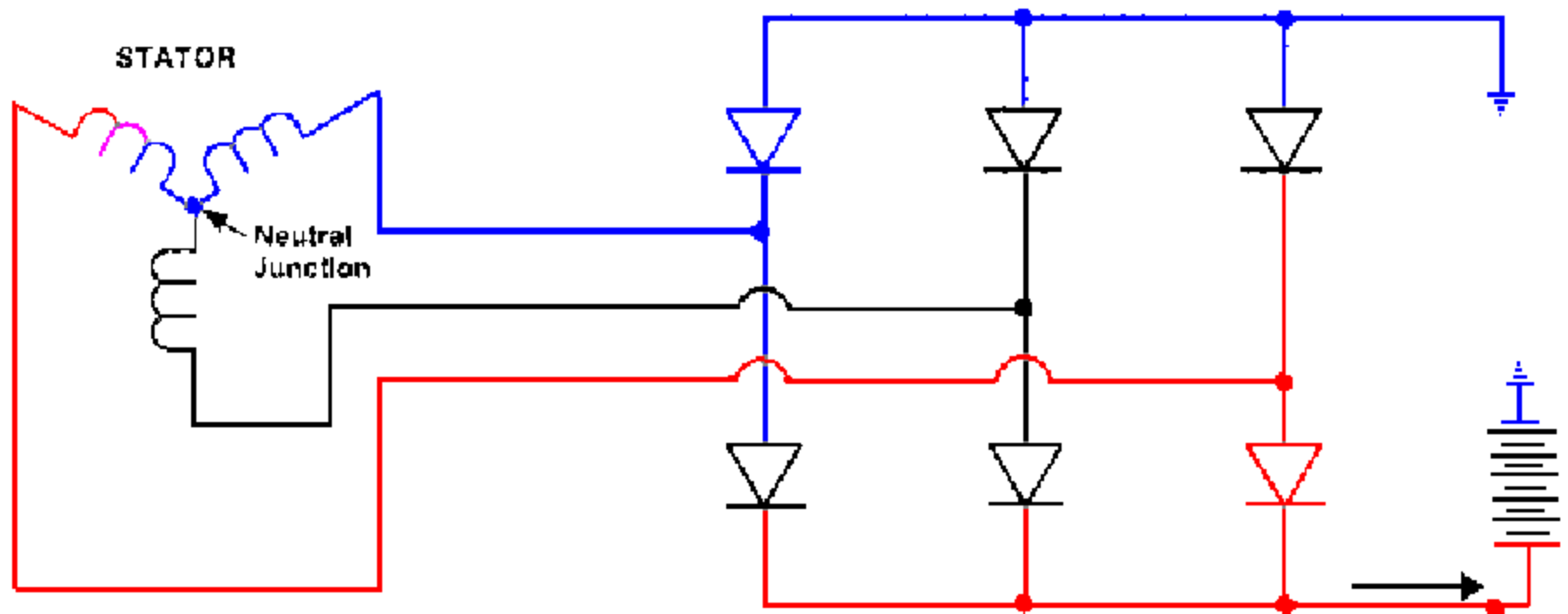Full Wave Rectification ...  
... one stator winding



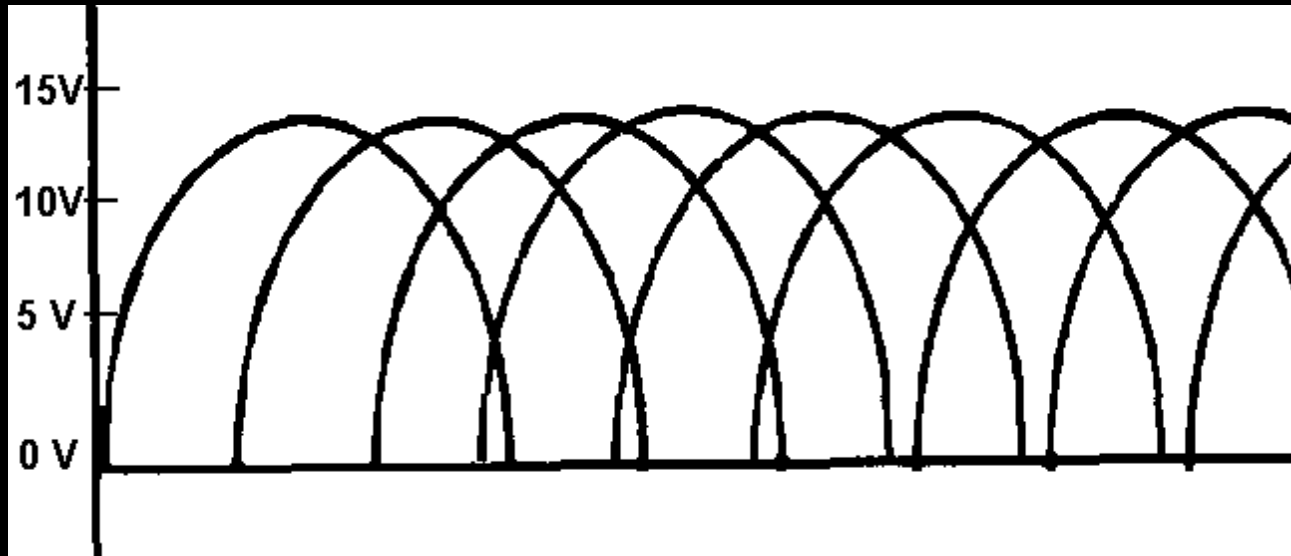Full Wave Rectification ...  
... three stator windings



Actual voltage trace of each stator winding after full wave rectification



voltage trace on oscilloscope  
(diode pattern)



Stator

Rectifier  
(Diode pack)






Positive Diode  
Heat-sink

Negative Diode  
Heat-sink

B+  
Main Charge  
Terminal

Stator Wires


Voltage  
Regulator

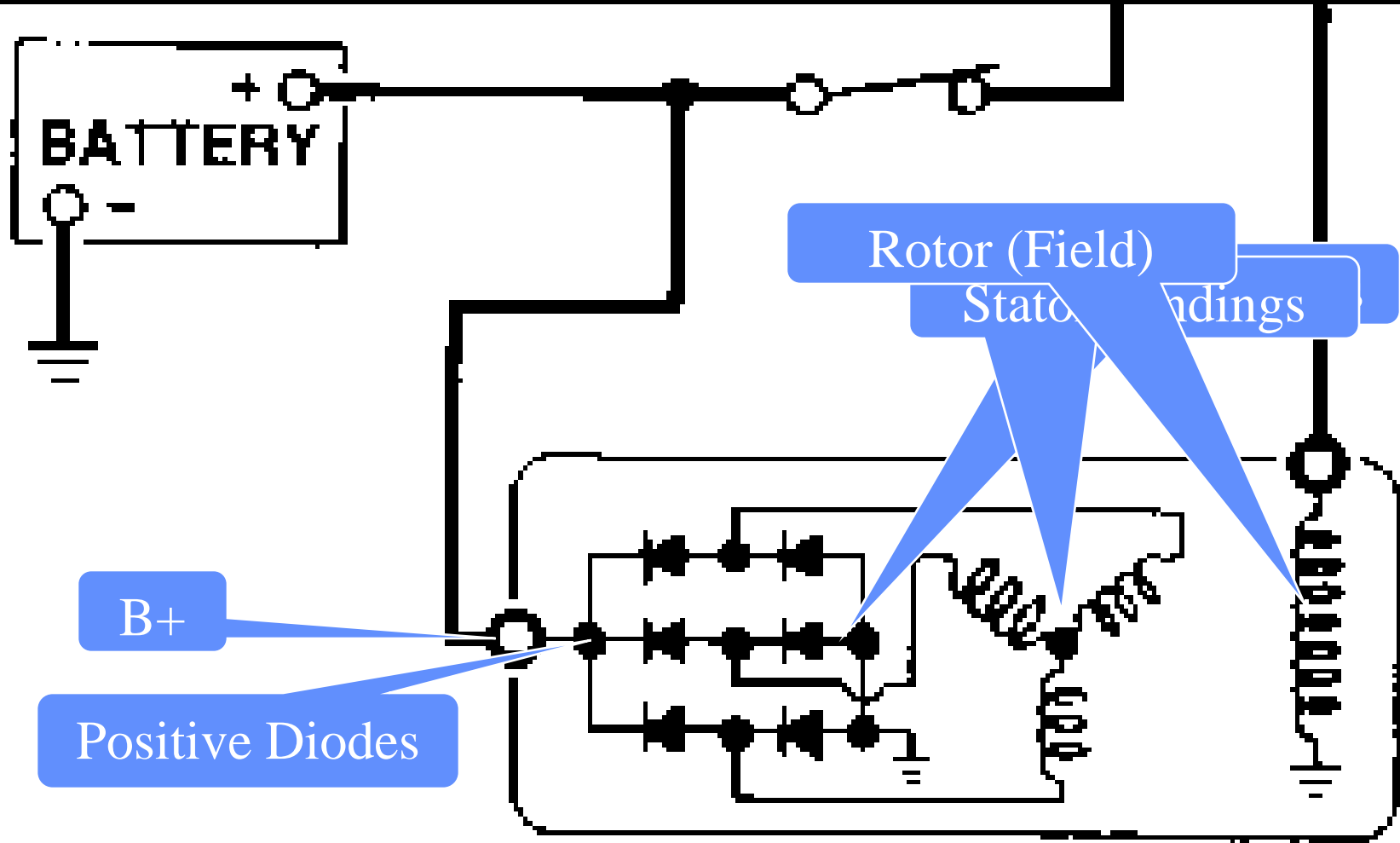


Test the electrical integrity of the diodes

Use an A/C voltmeter, or oscilloscope while the alternator is loaded

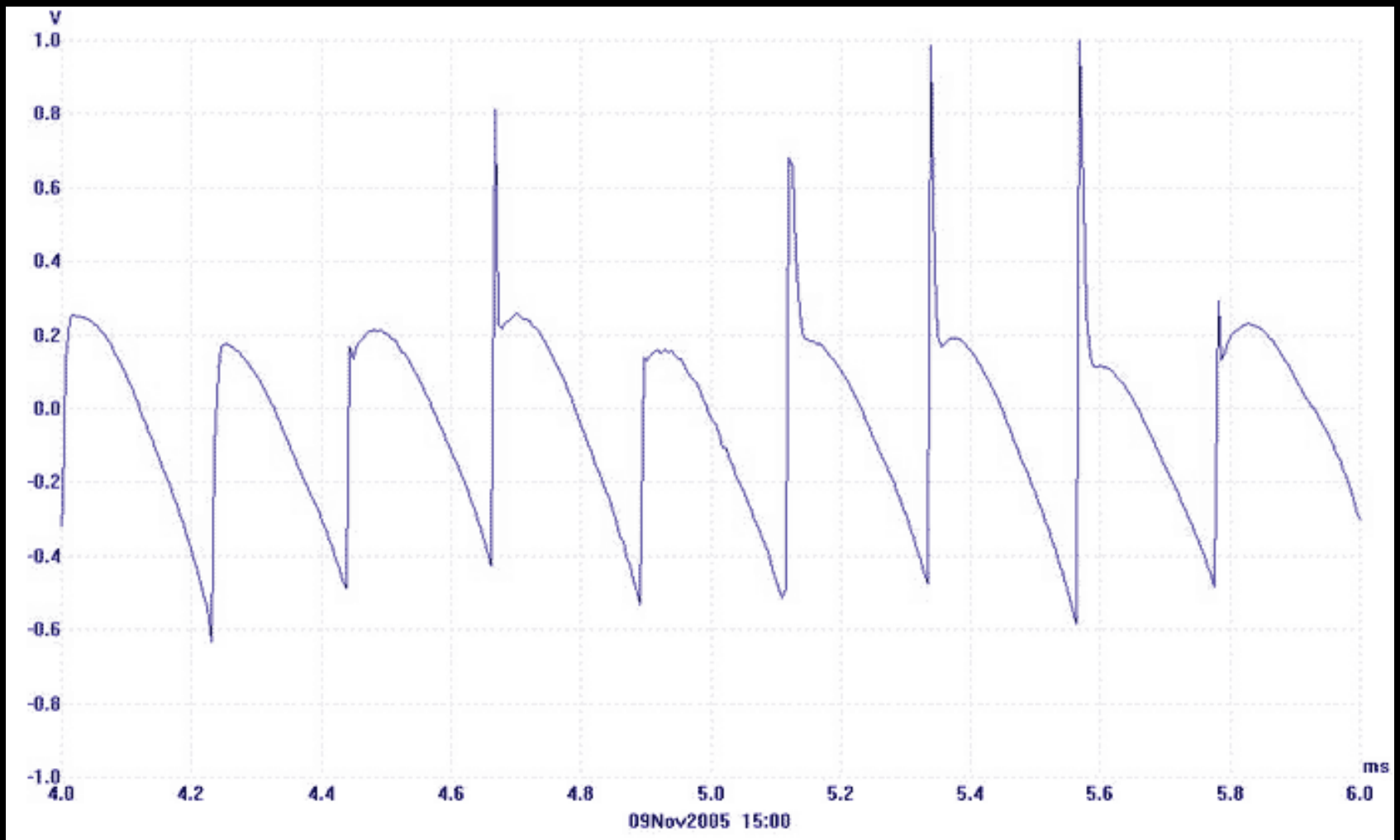
Turn on accessories, or put 40 amp draw on carbon pile



Here is a normal diode pattern

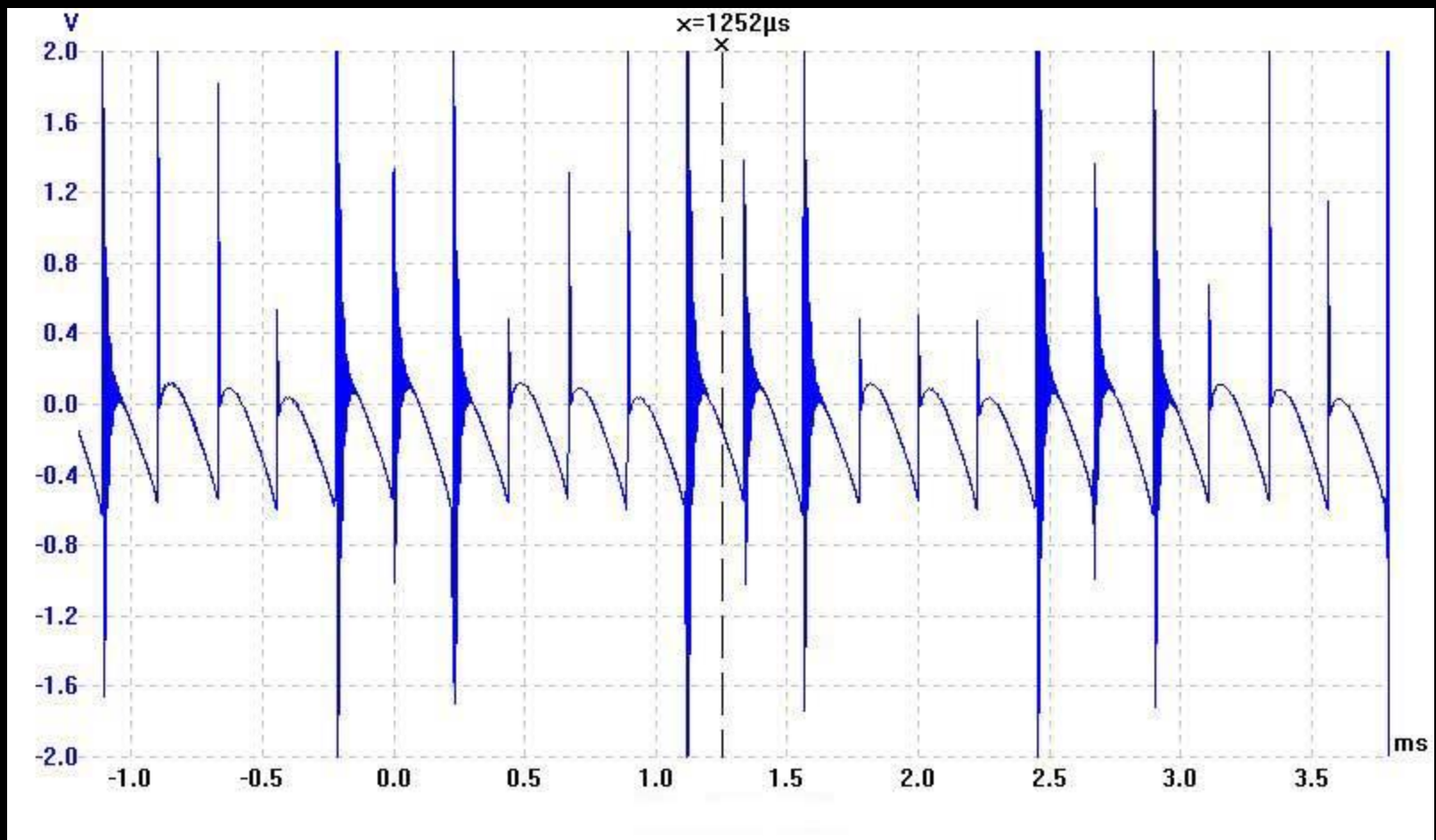


Here is a normal diode pattern

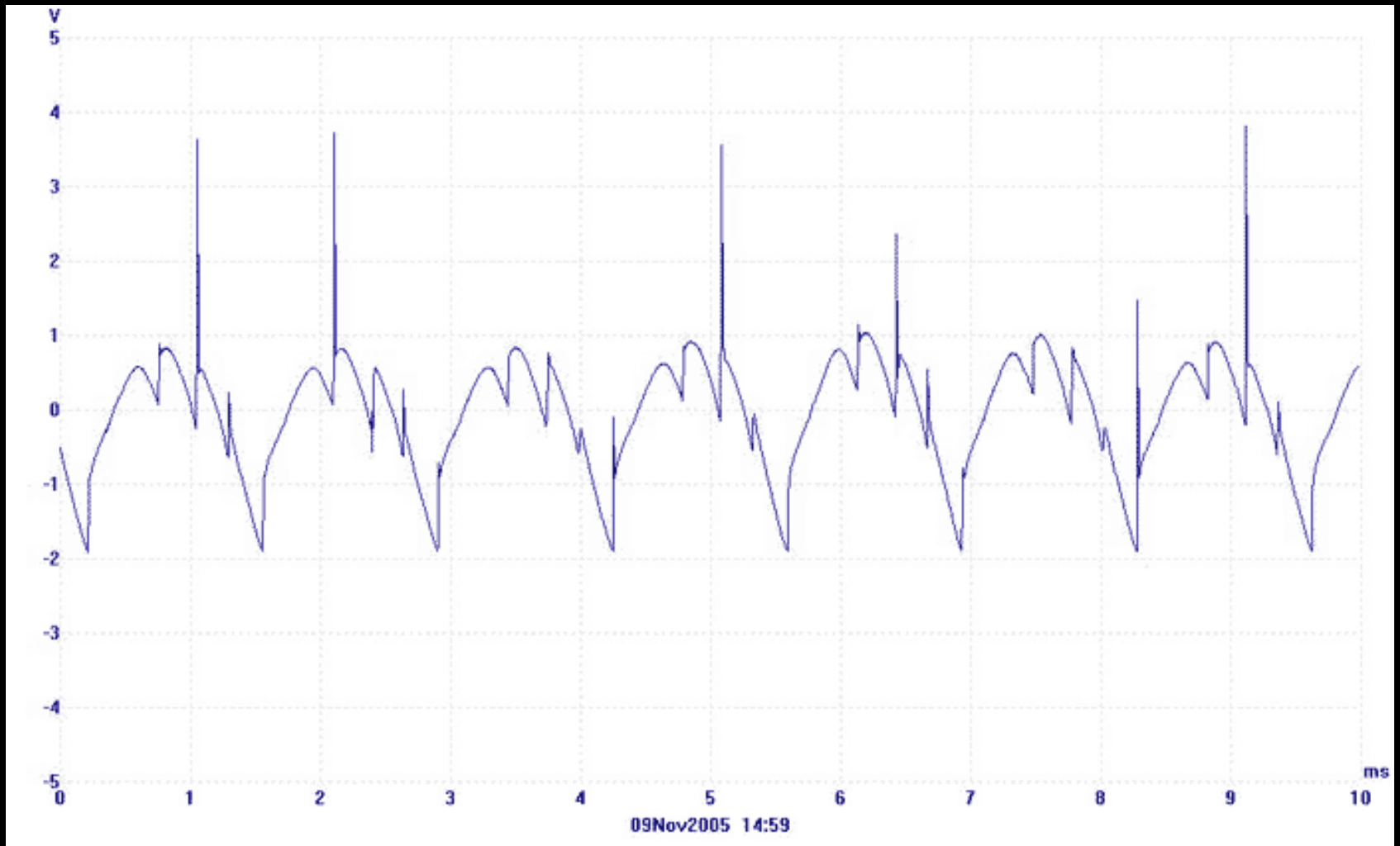


Open diode pattern



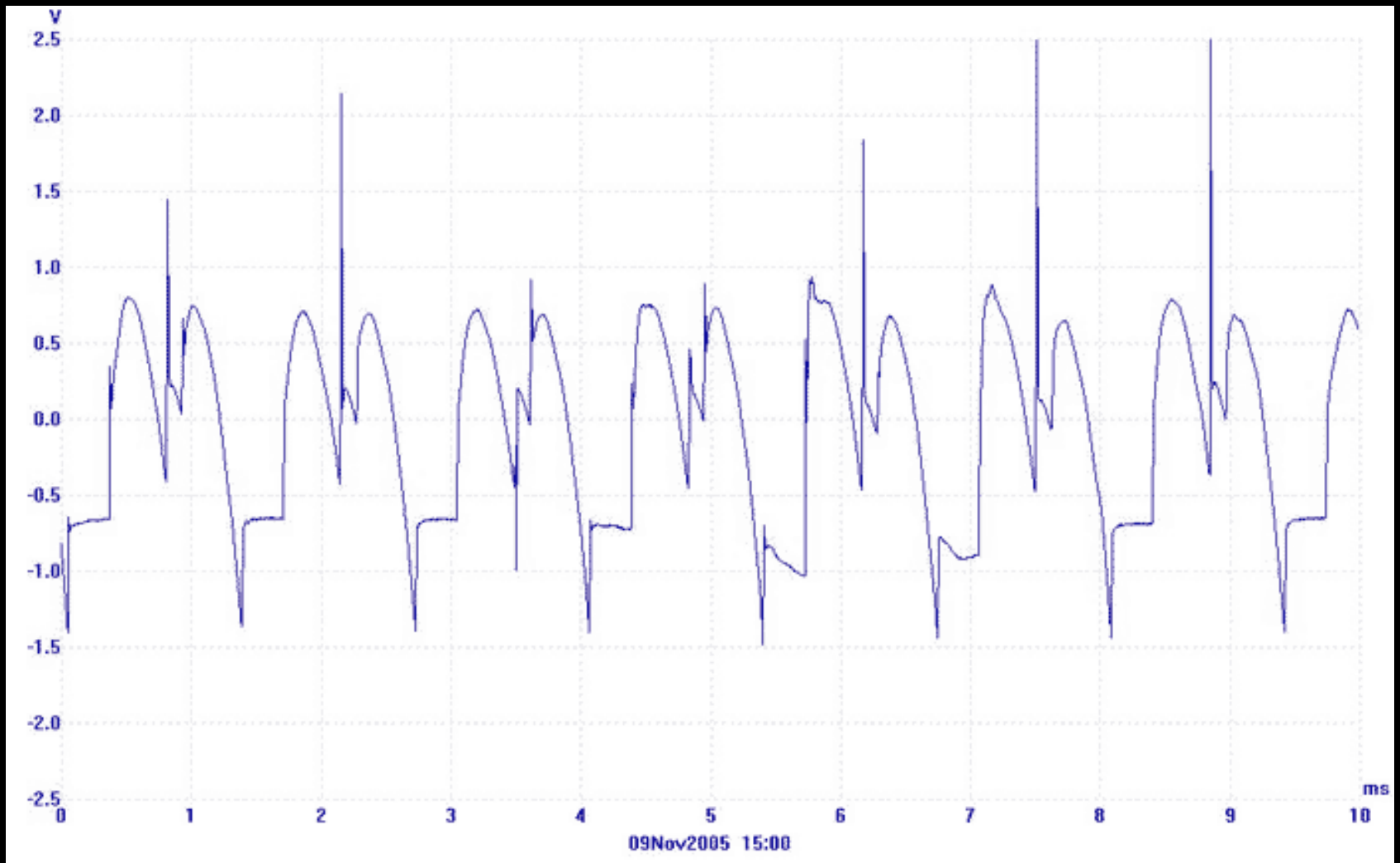

Shorted diode pattern

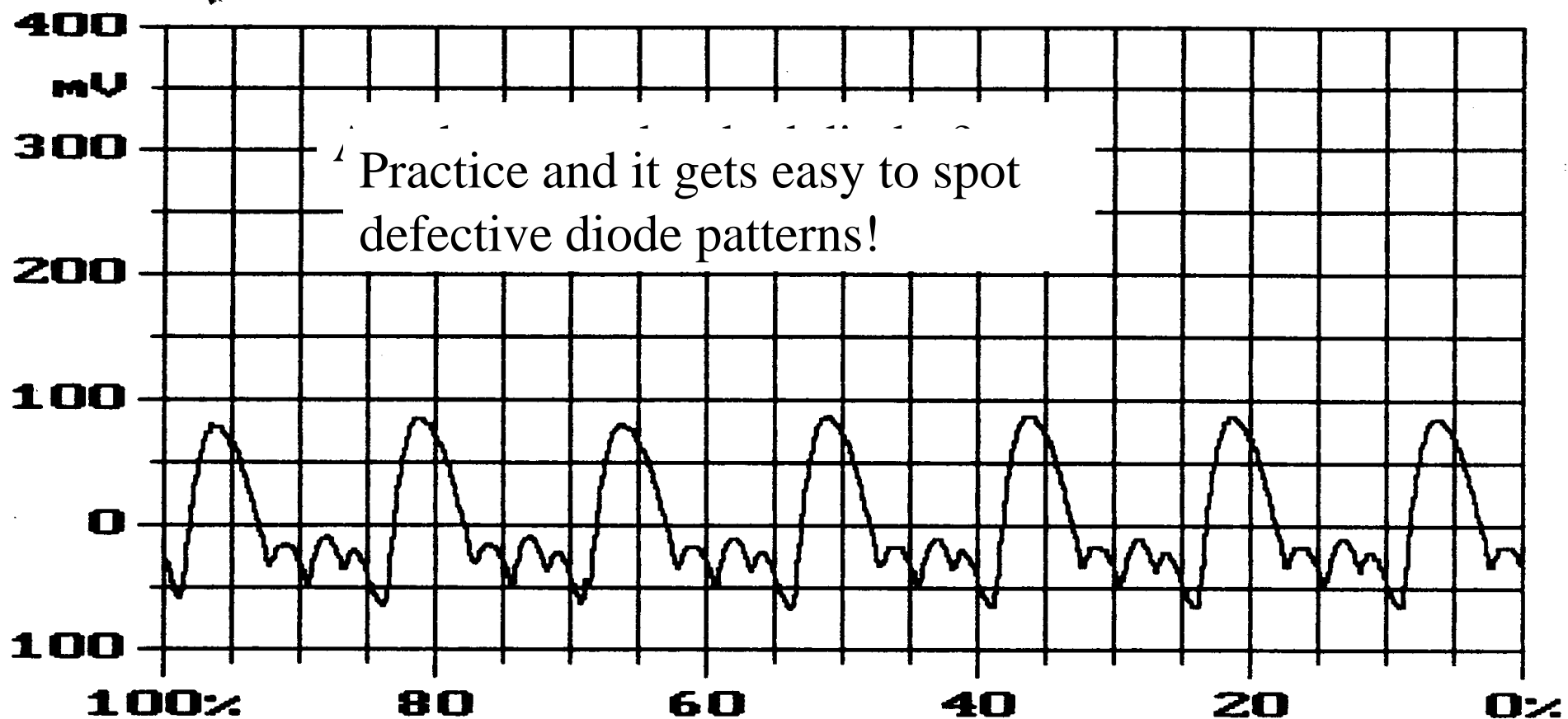

> Press MENU for SETUP selections  
> Press ENTER for REFERENCE mode  
> Press CONTINUE for PINPOINT

Scope set for A/C voltage

# Practice with Diode Patterns

- Different alternator diodes give slightly different diode patterns
- If you look at many different alternator diode patterns you will learn to quickly spot bad diodes
- Defective diodes can cause many engine performance problems
- Do not forget to load the system


# How can you increase the amperage coming out of the generator?

Increase engine RPM

(This is limited to about 2500 RPM)


Increase the rotor's magnetic field strength

Use a Delta stator winding

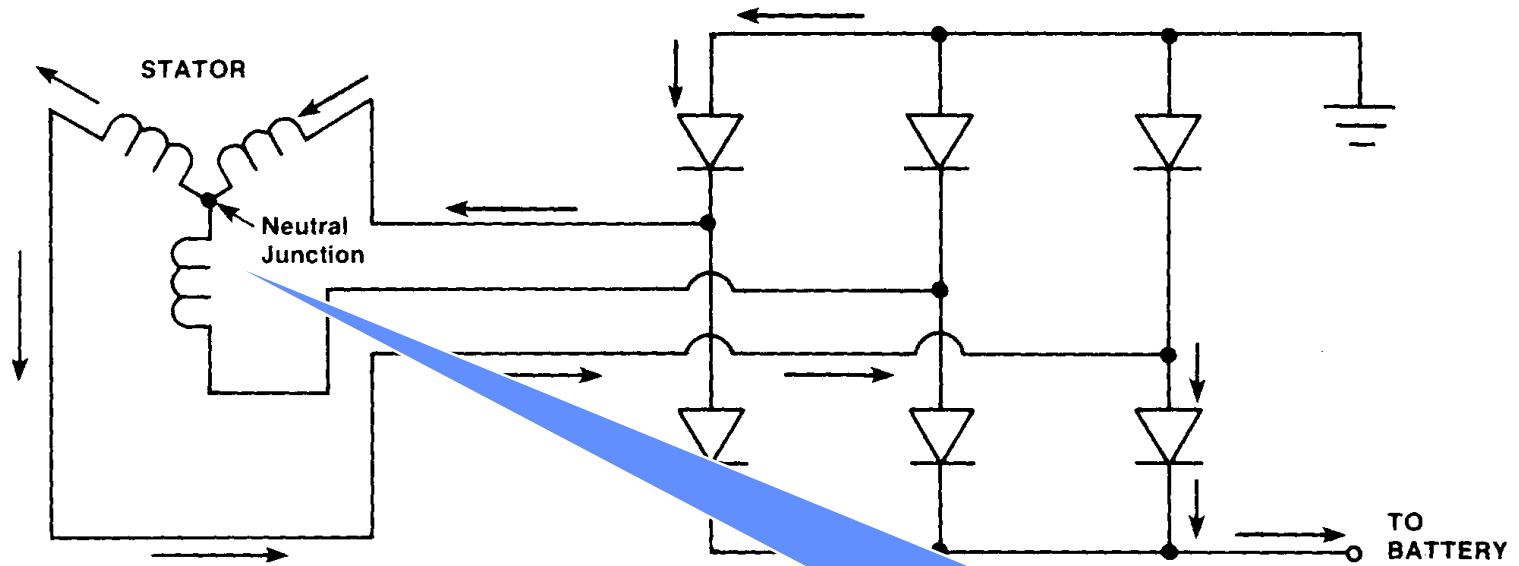

**Figure 10-13** Wye stator wired to six diodes

Delta stator = higher output

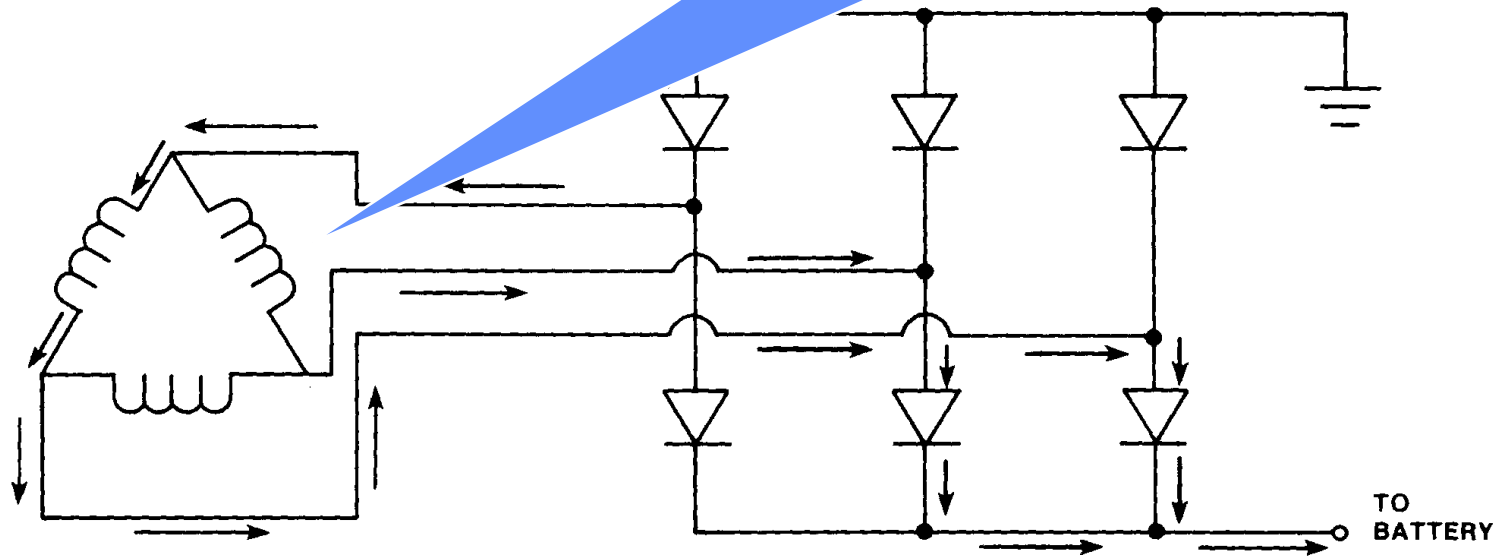

**Figure 10-14** Delta stator wired to six diodes

# How does the voltage regulator control the A/C generator?

The regulator will turn on/off current to the field windings (rotor)


Increasing current to the rotor...  
...will increase generator output



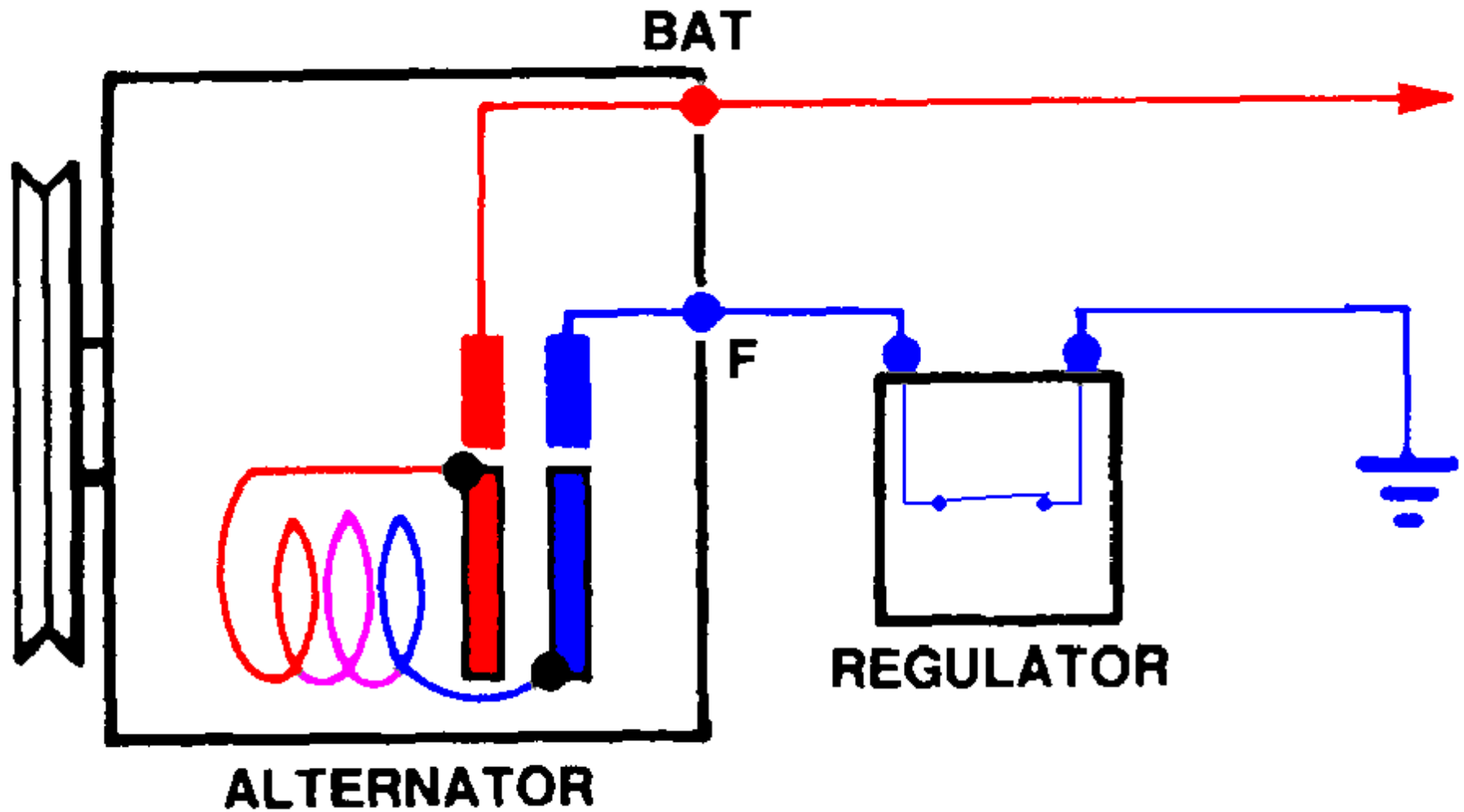
# How does the voltage regulator control the A/C generator?

Regulators are wired to the Ground side of the Rotor in an A type circuit


and wired to the Battery side of the Rotor in a B type circuit




“A” circuit regulator

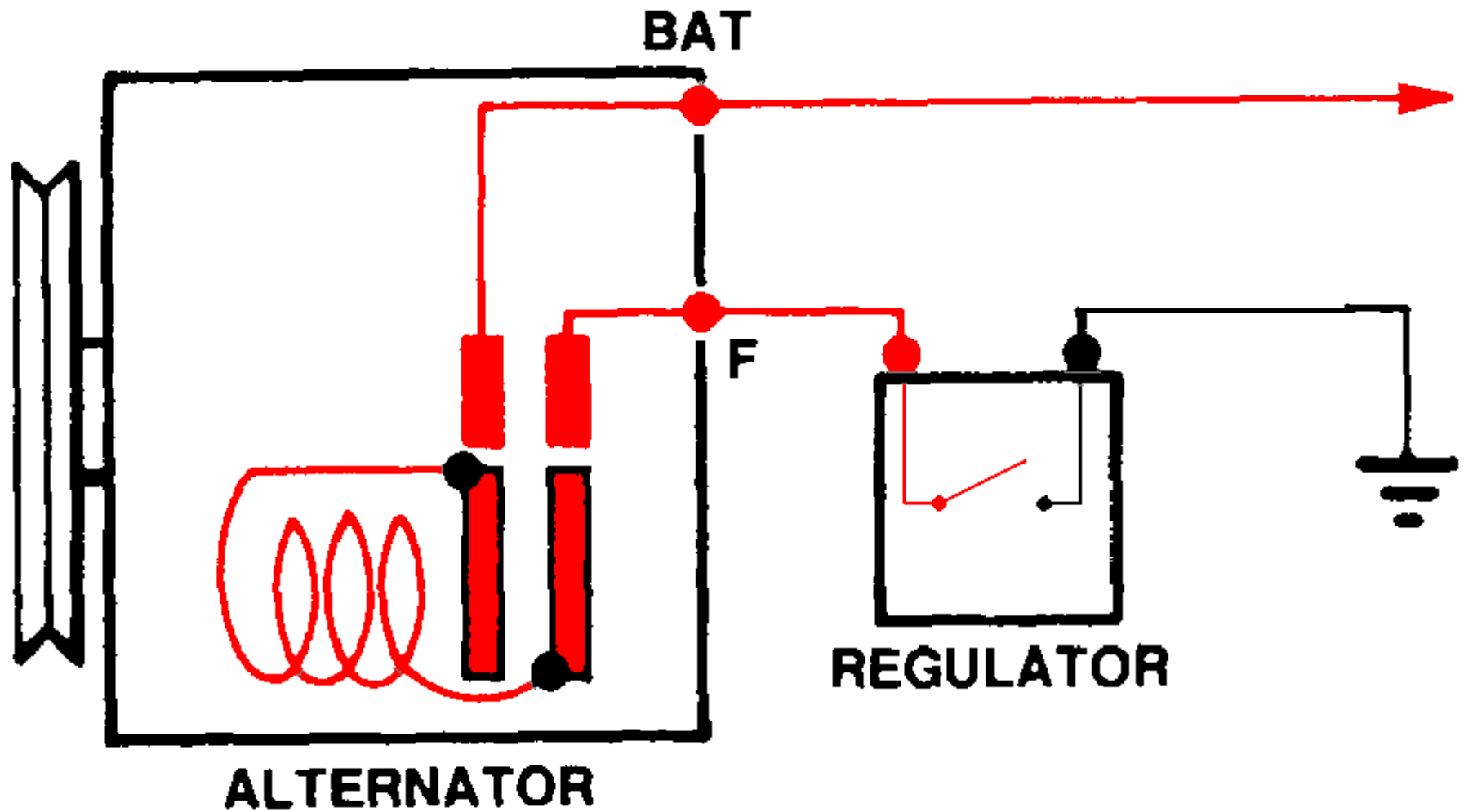

“A” circuit regulator

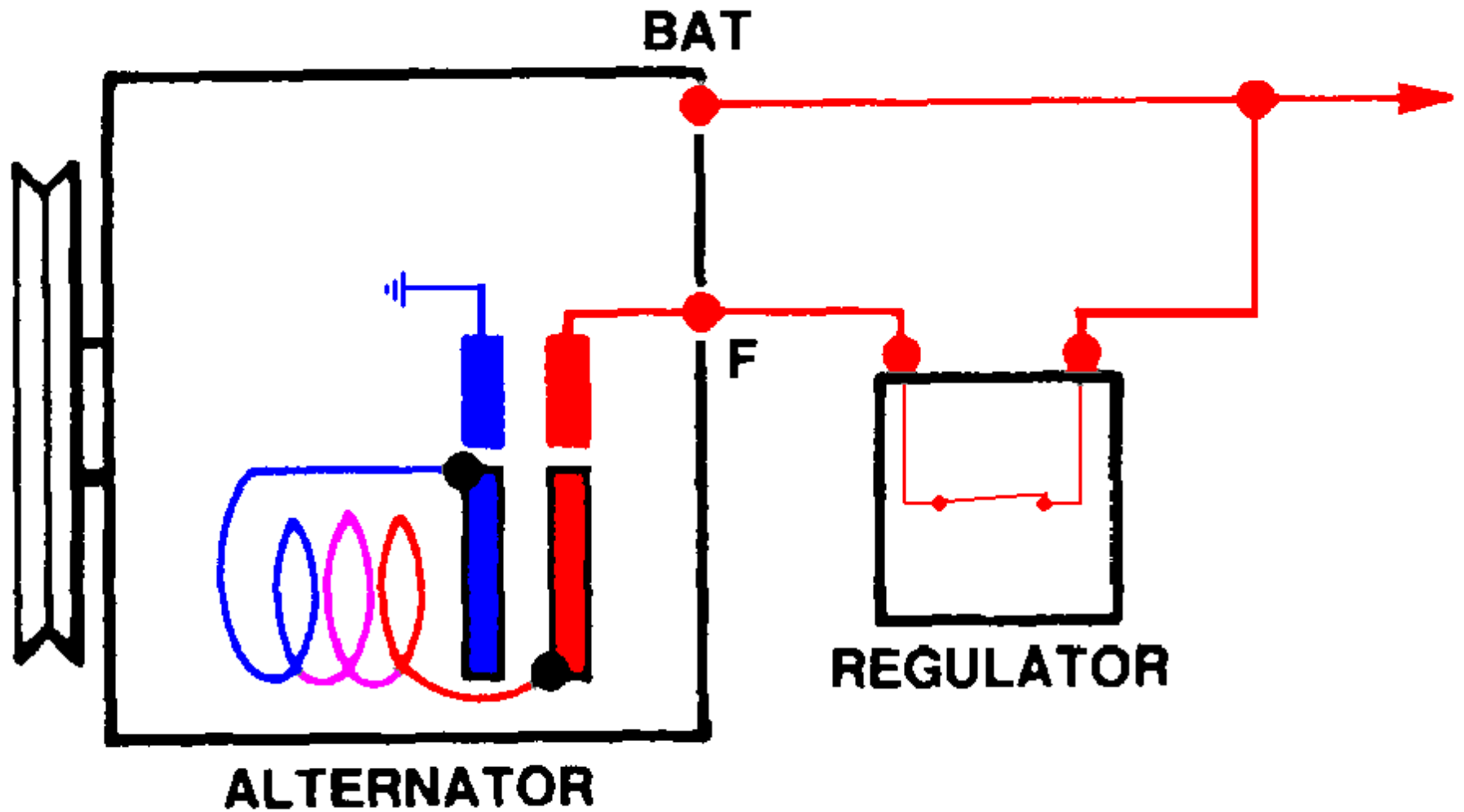

“B” circuit regulator

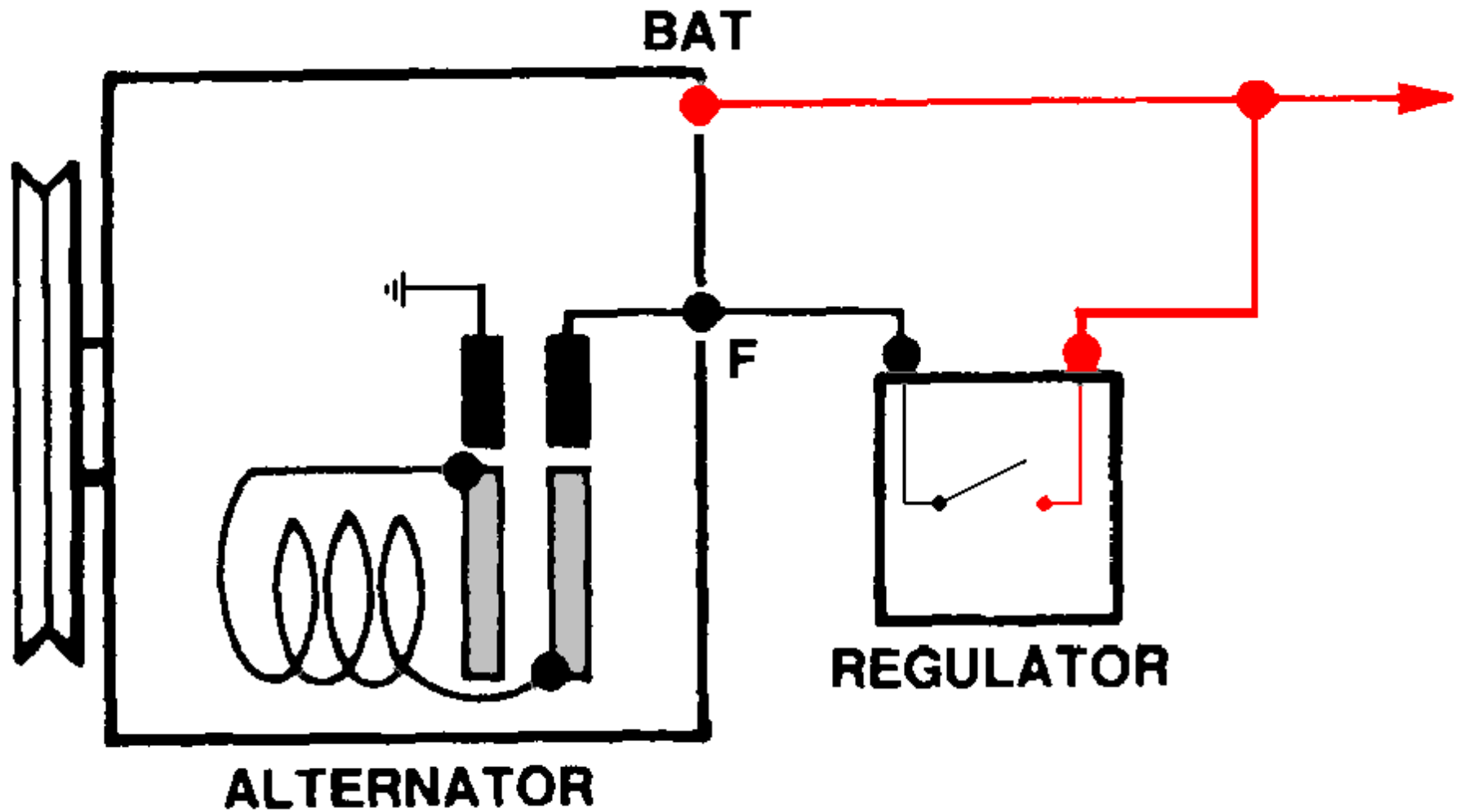


“B” circuit regulator


# Voltage regulators monitor


Voltage


Temperature



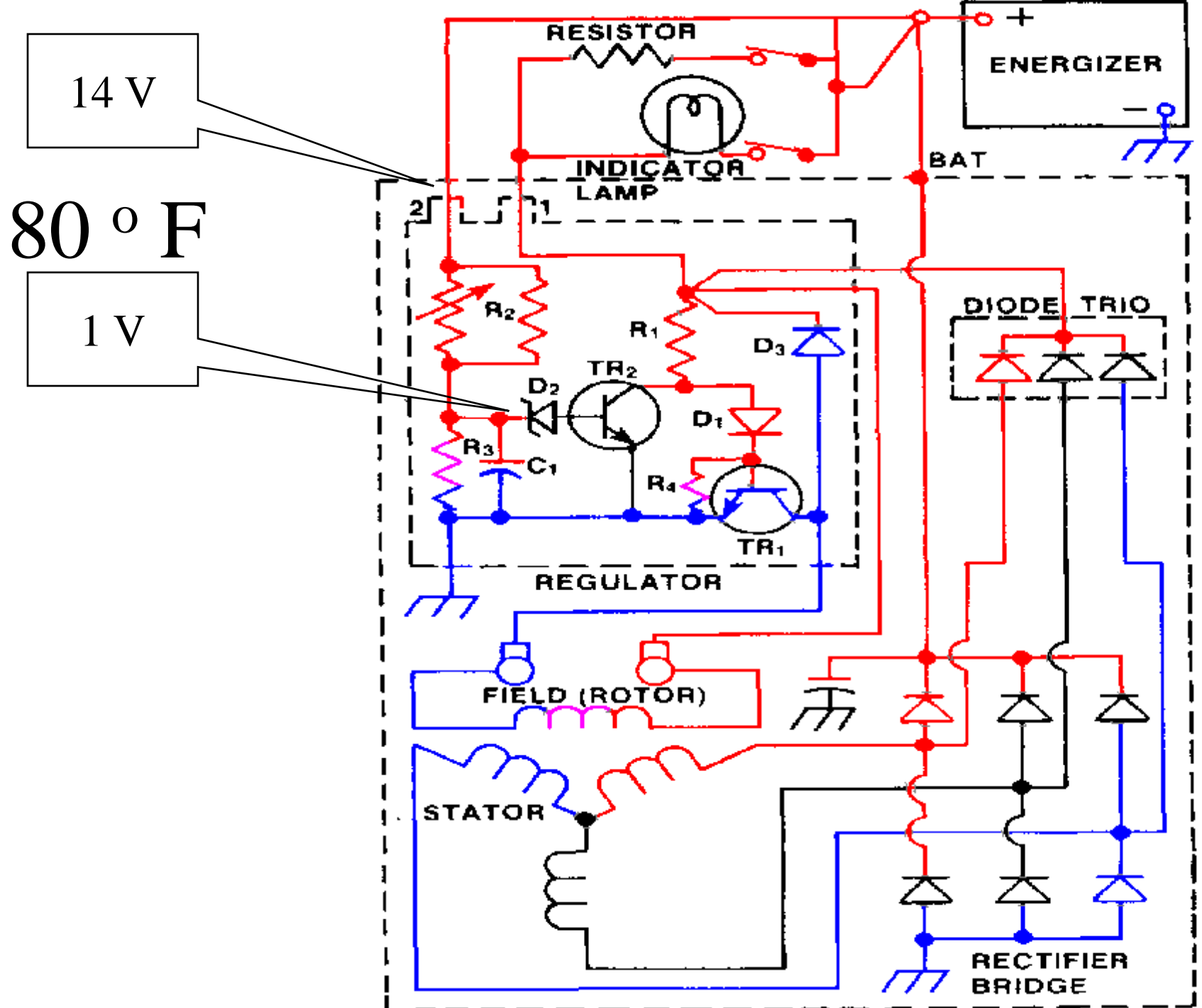

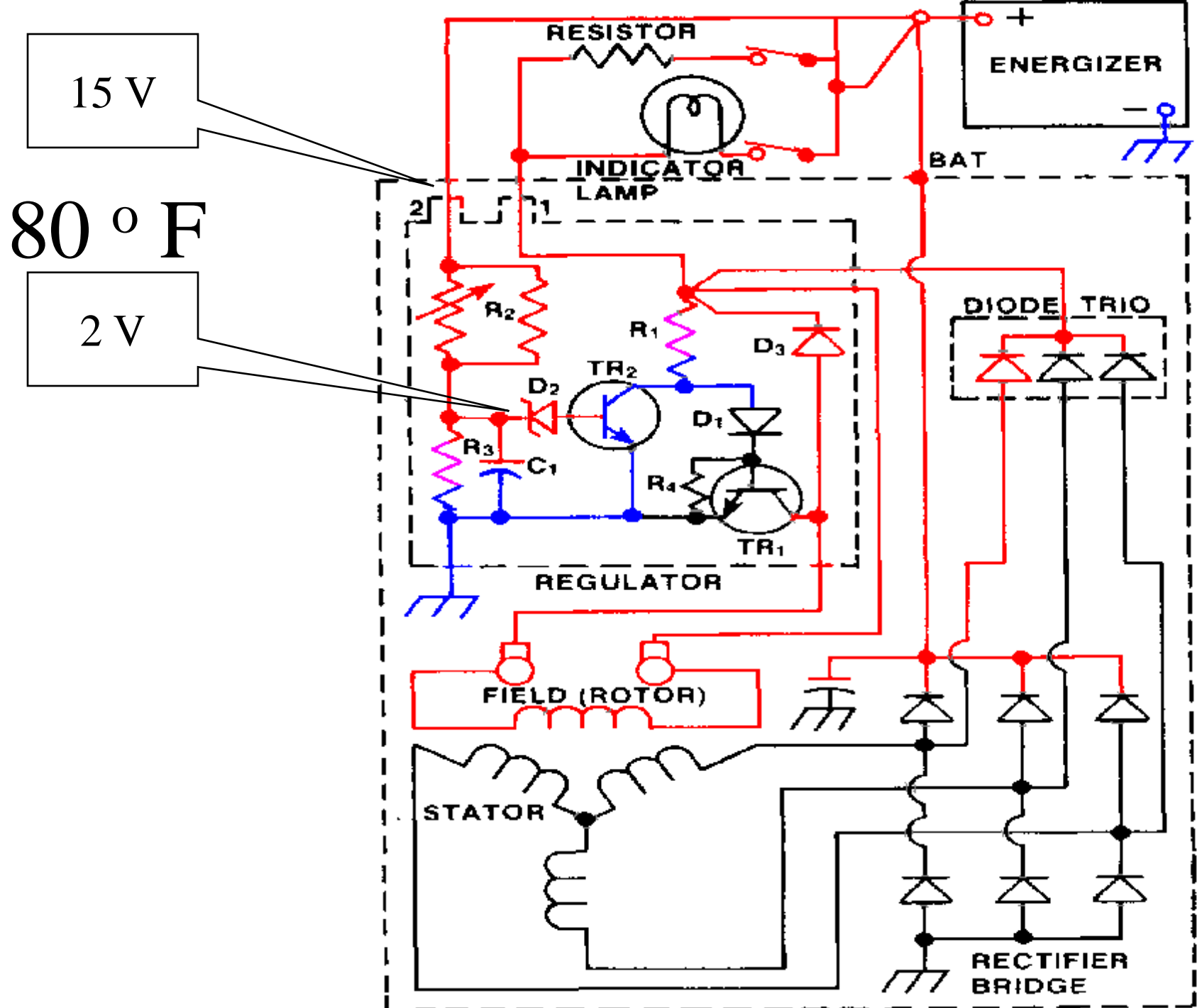

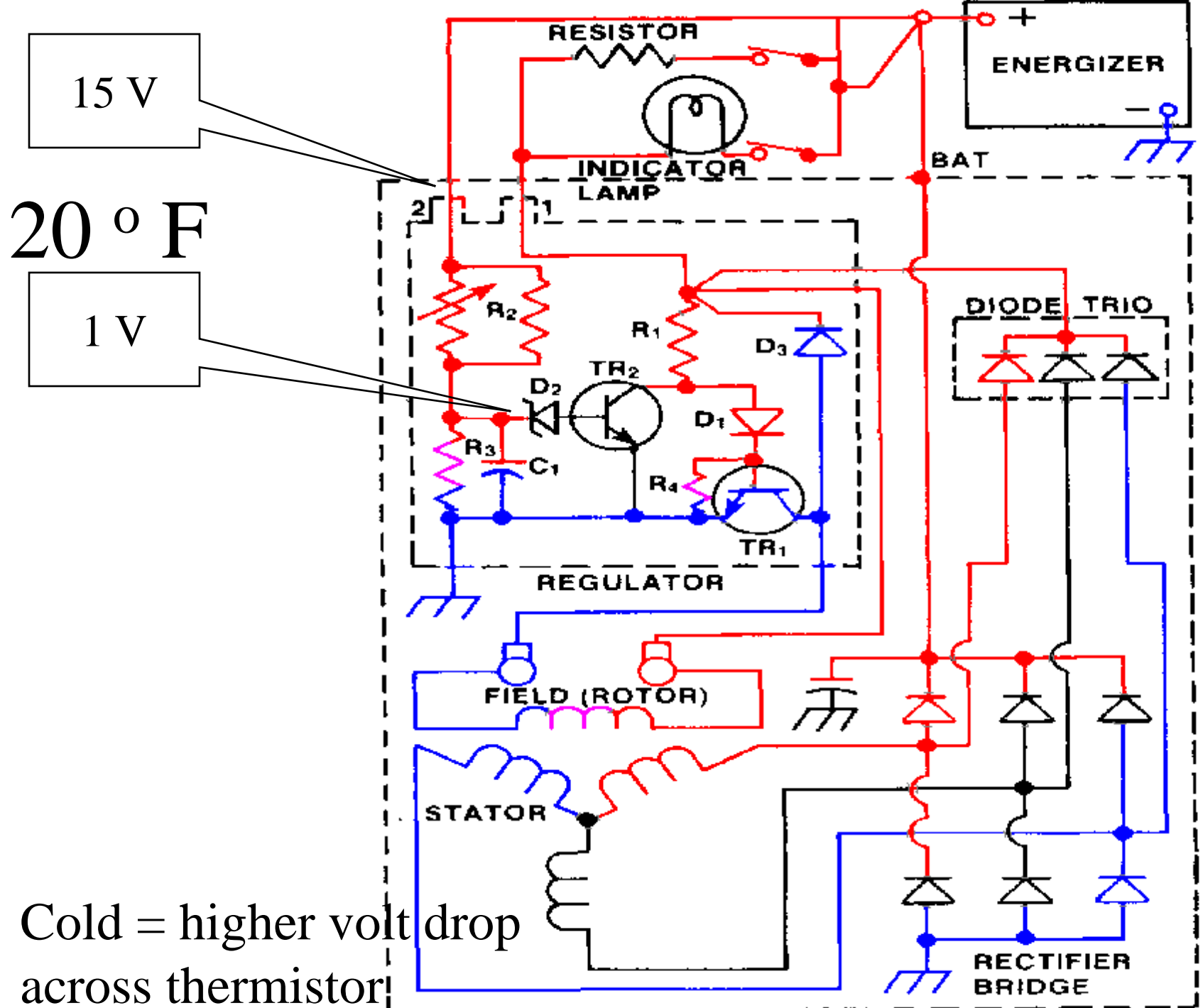

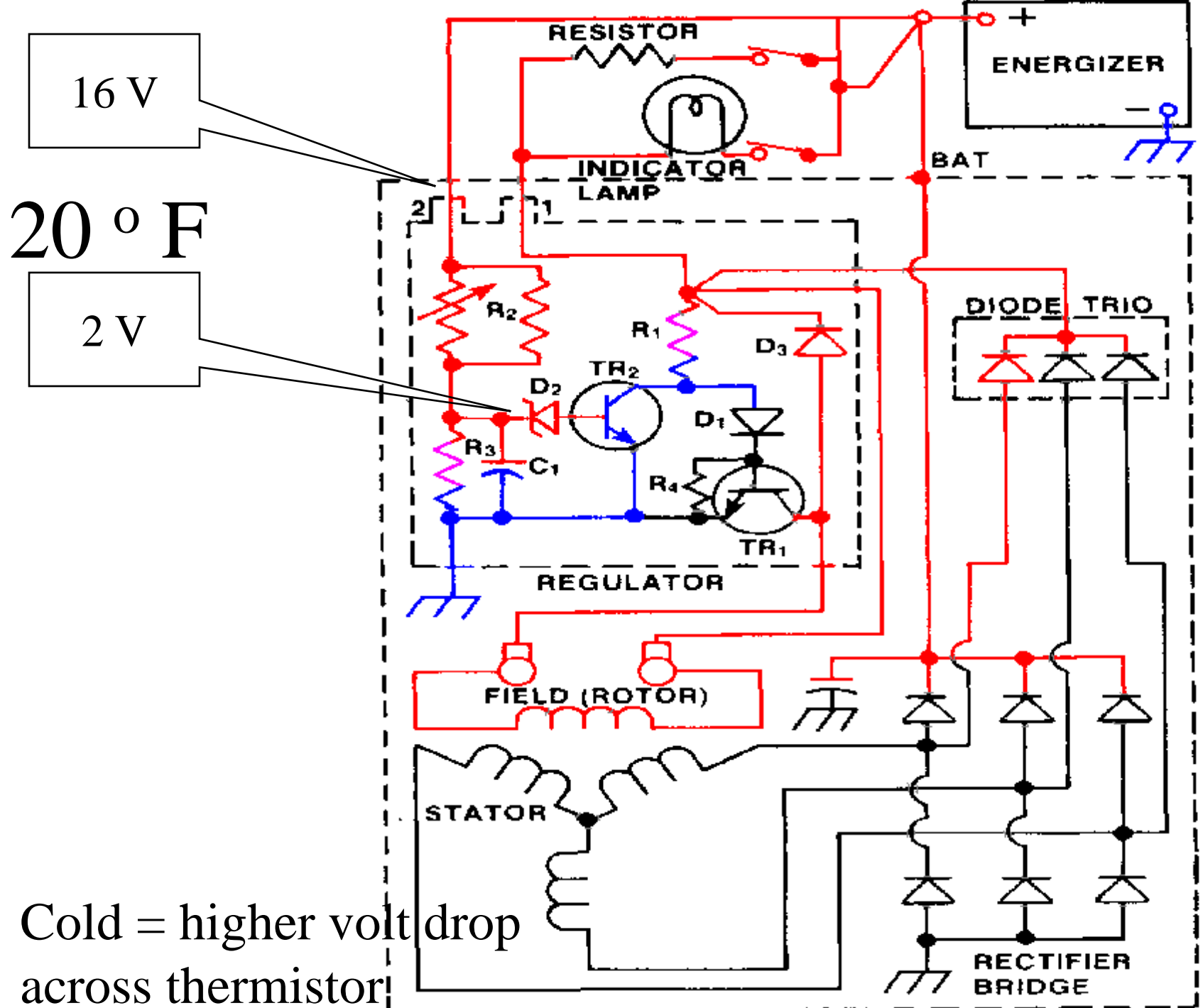



Voltage should:  
increase when cold,  
decrease when hot.


Explain how charging system indicators work

Idiot light



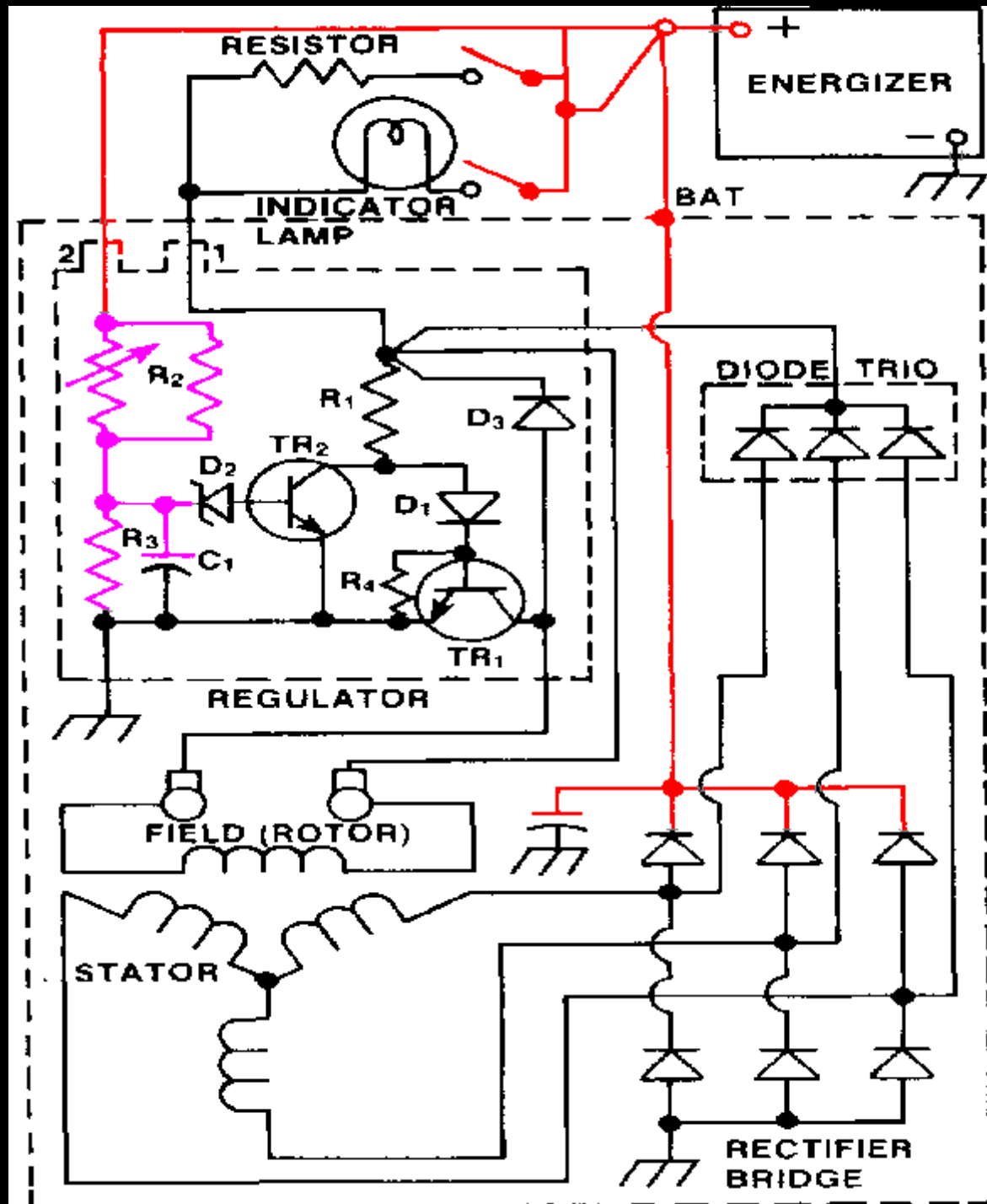

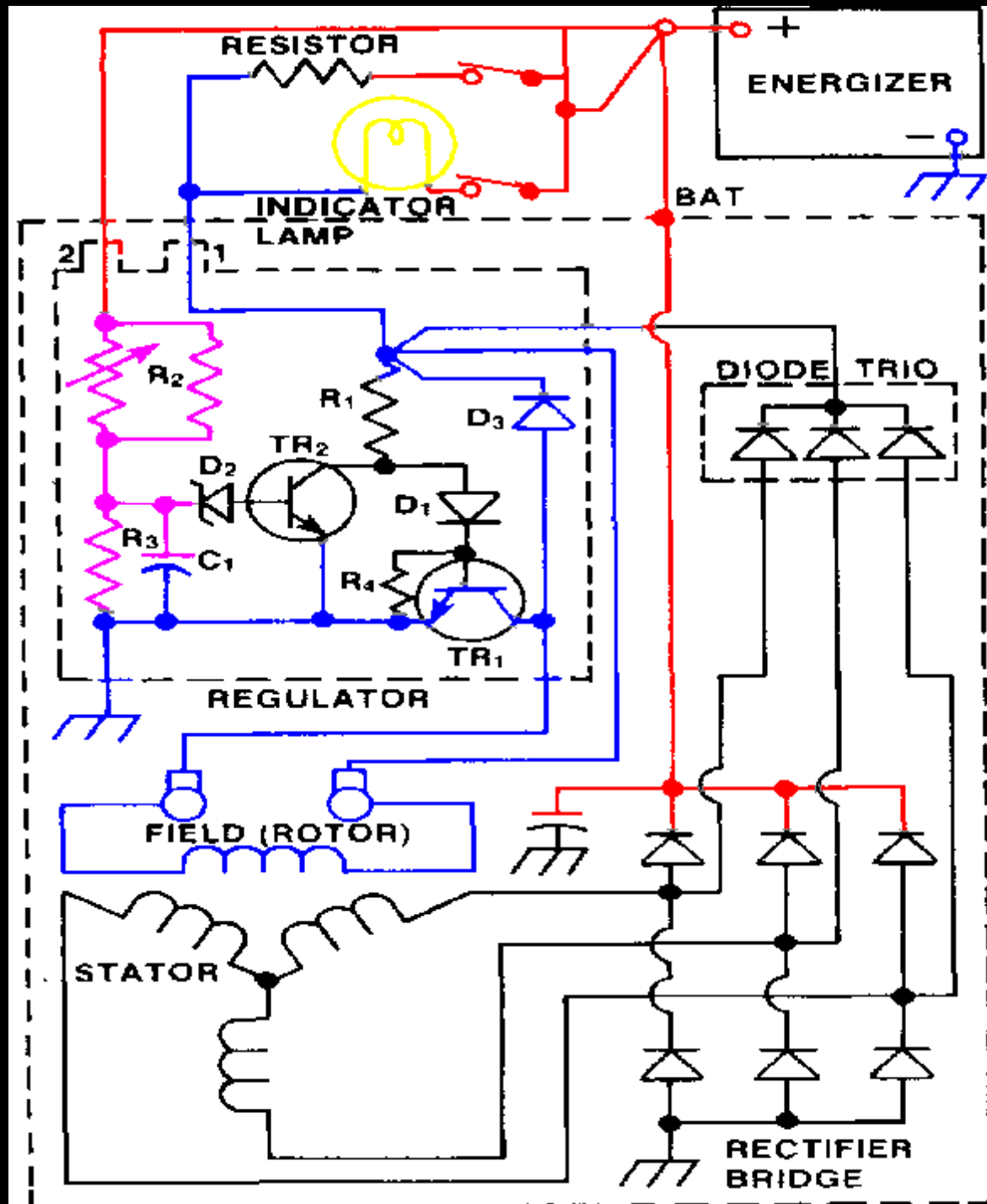

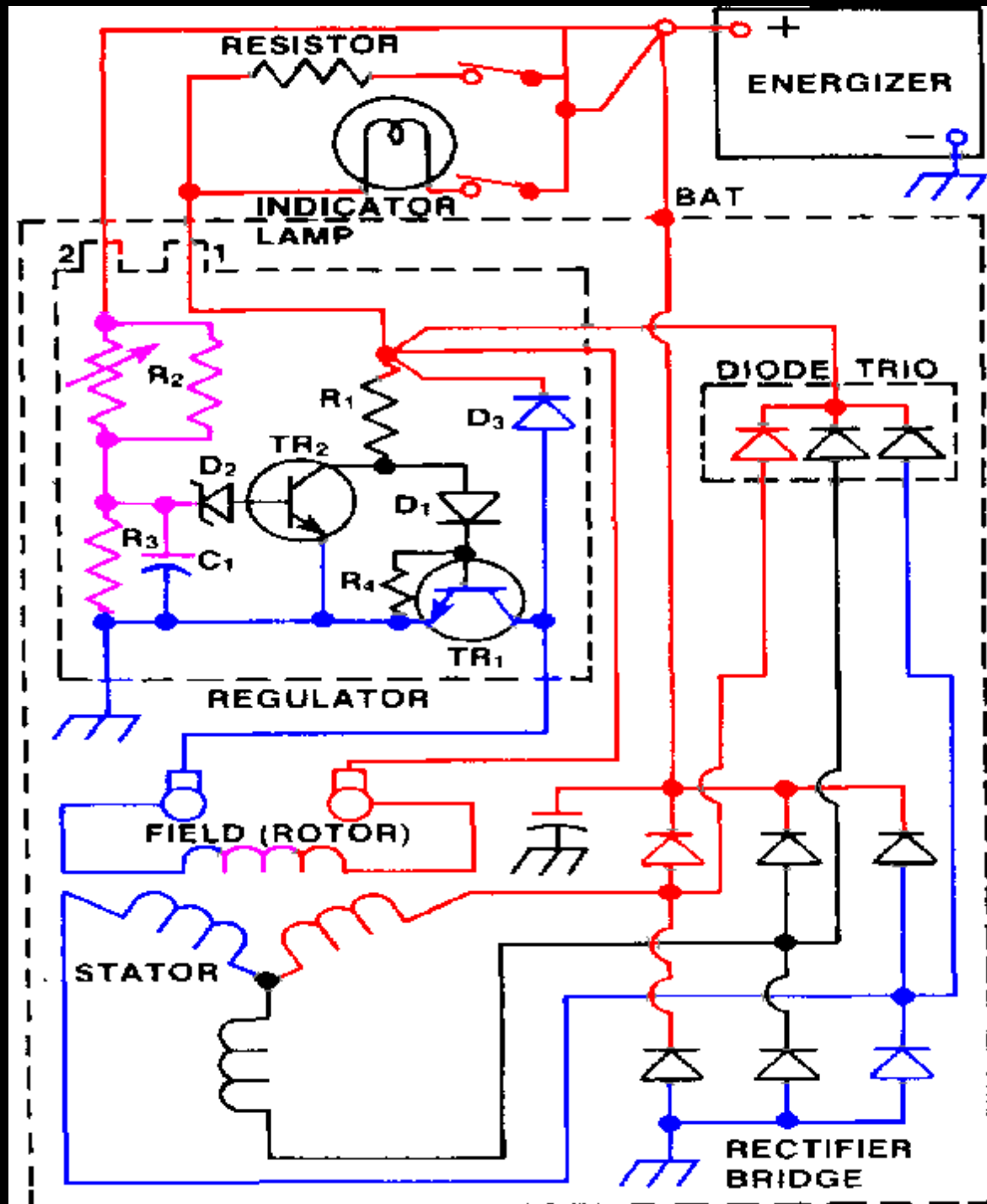


Explain how charging system indicators work

Idiot light

Voltmeter

Ammeter


# REGULATOR

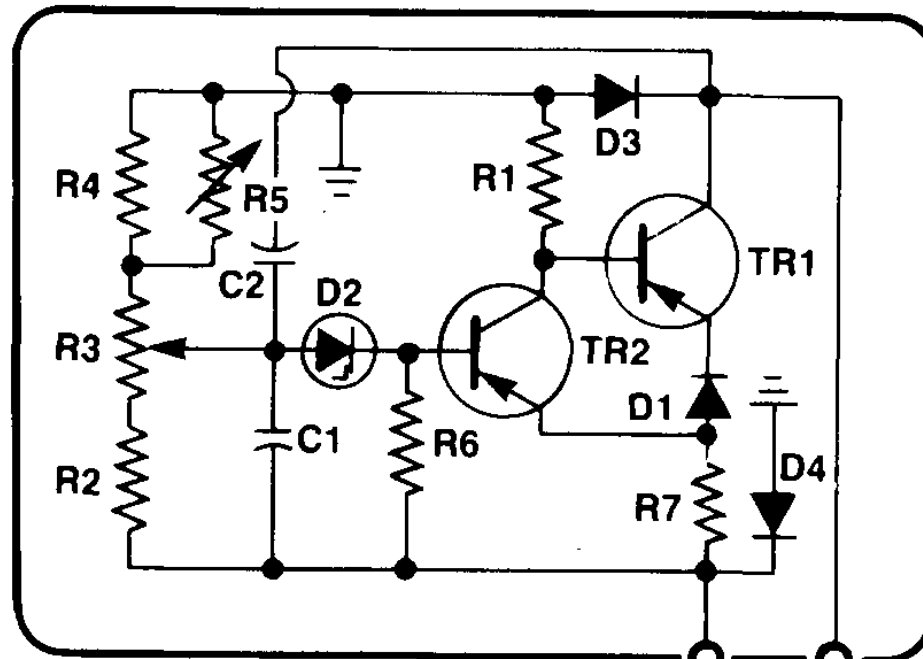


POS

F

AMMETER

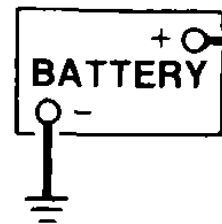

SWITCH

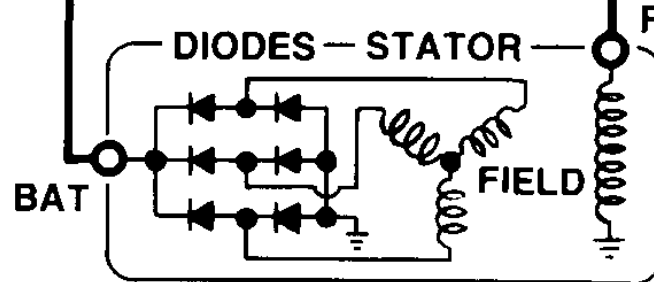

ALTERNATOR

# Diagnose Over/Under Charging

Insure there is no Voltage drop in wiring harness



Undercharge is bad alternator or regulator

Overcharge is bad regulator


IF there are no bad wires or connections




## REGULATOR

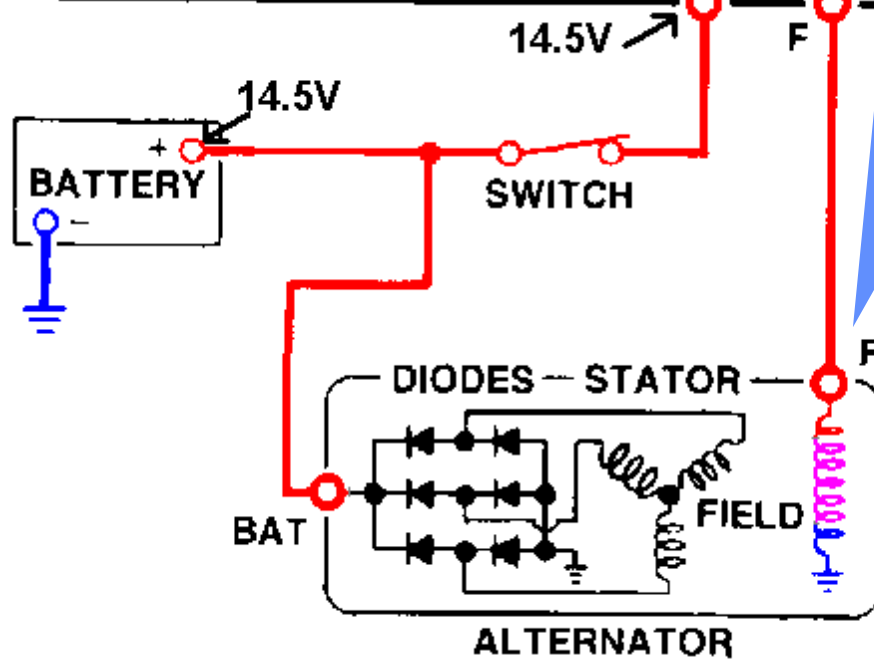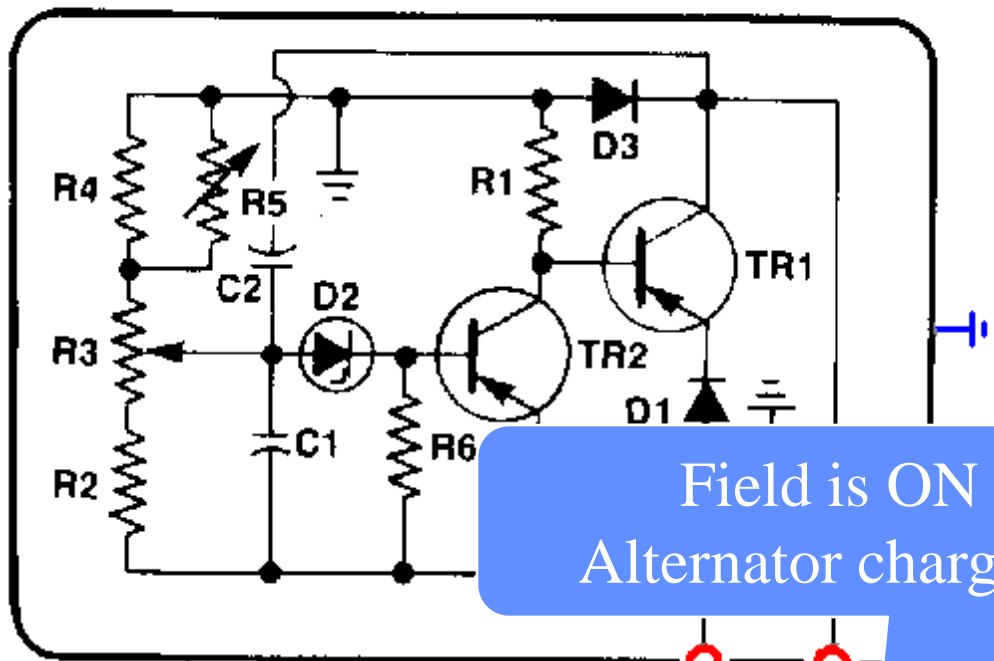


## REGULATOR

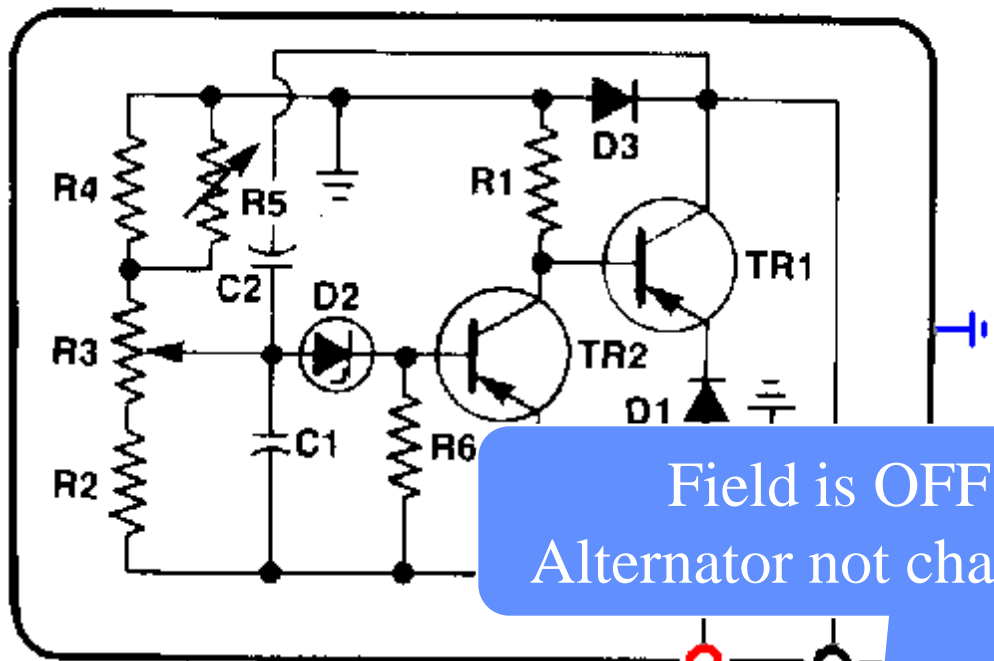

Field is OFF  
Alternator not charging

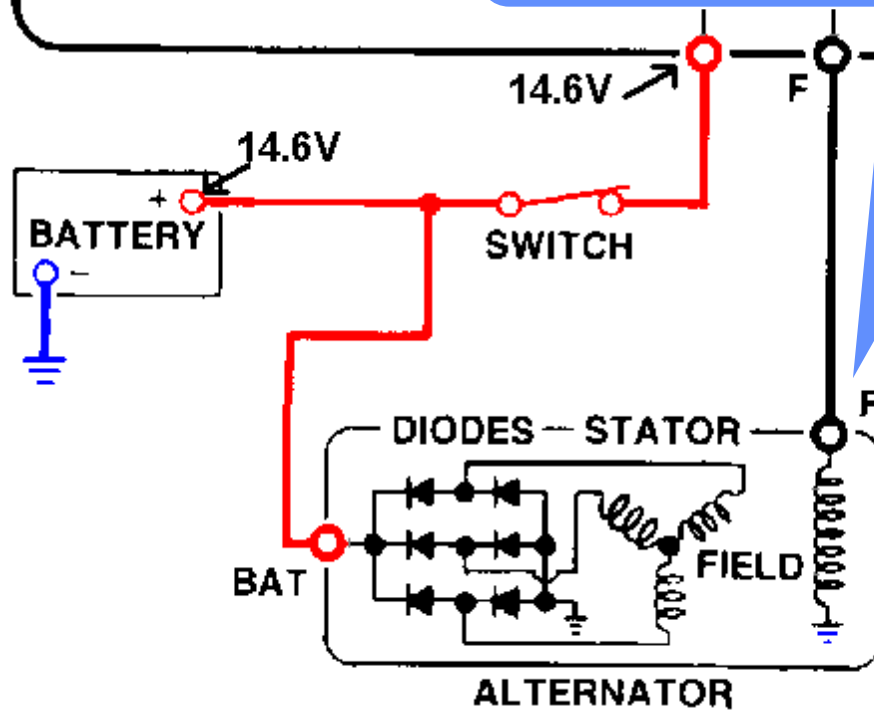


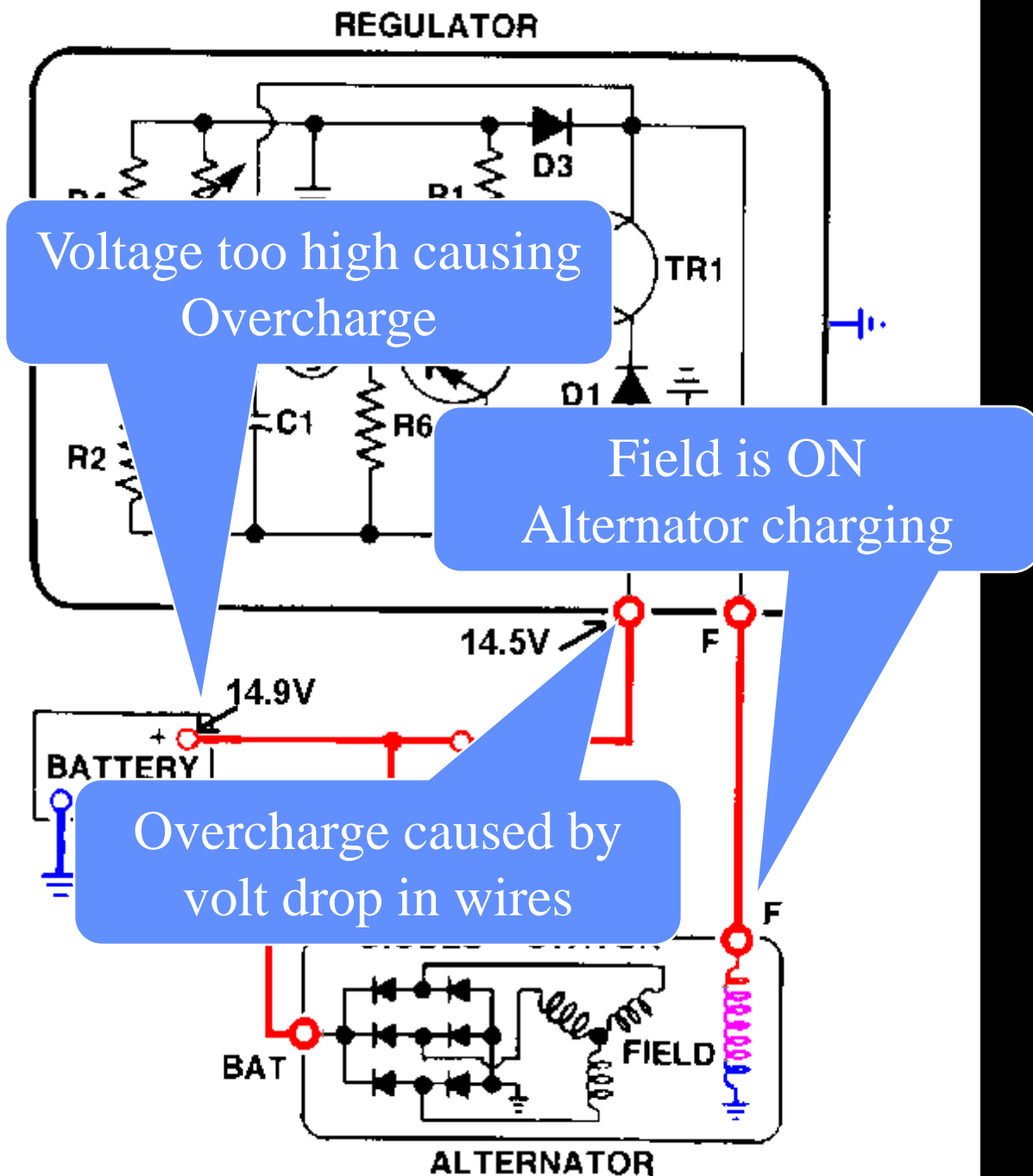

Regulator only “sees” 14.5 volts

Voltage too high  
Overcharge

Field is ON  
Alternator charging

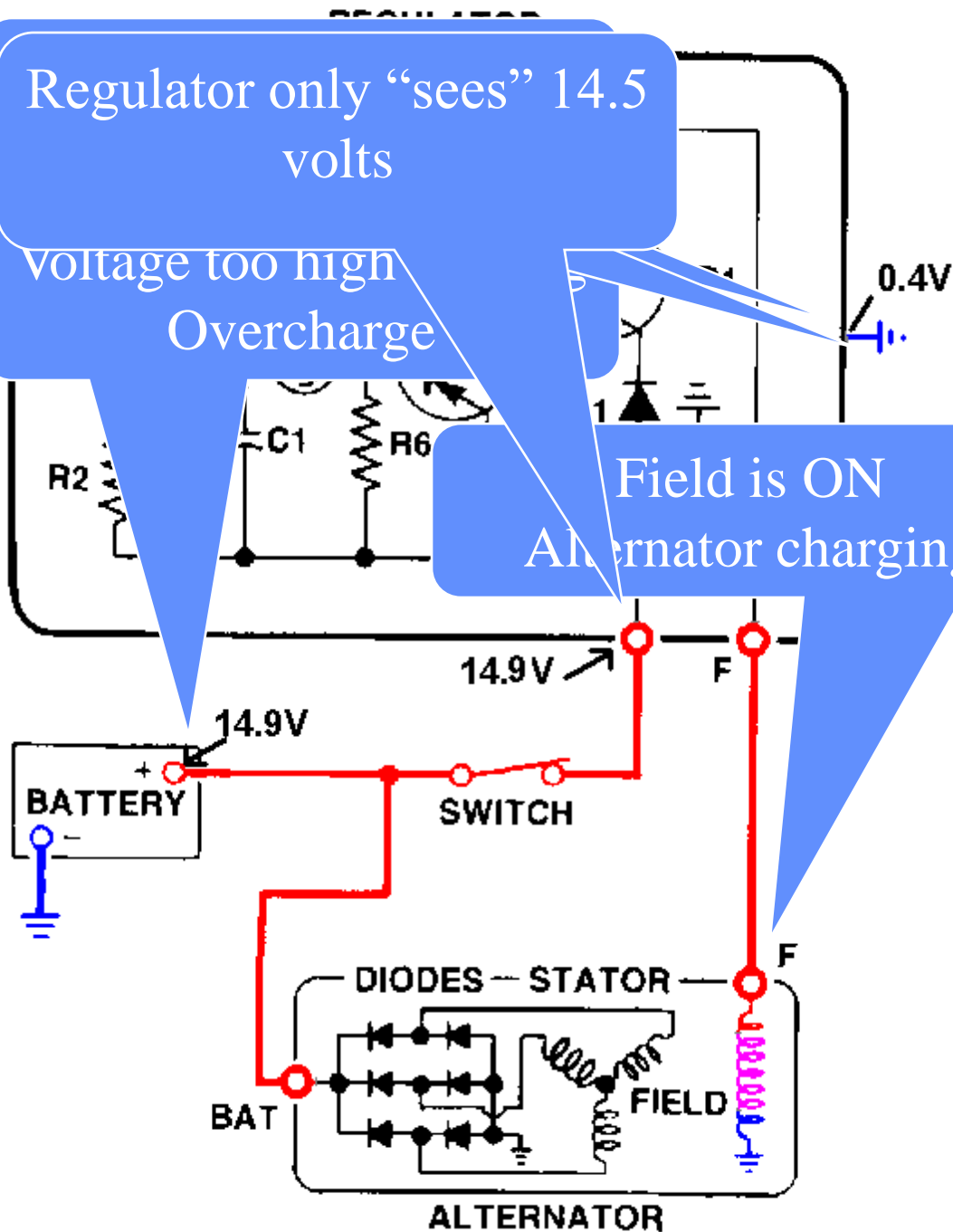


## REGULATOR

Regulator “sees”

Volt Drop in battery cables will  
cause undercharging

Field is OFF  
Alternator not charging

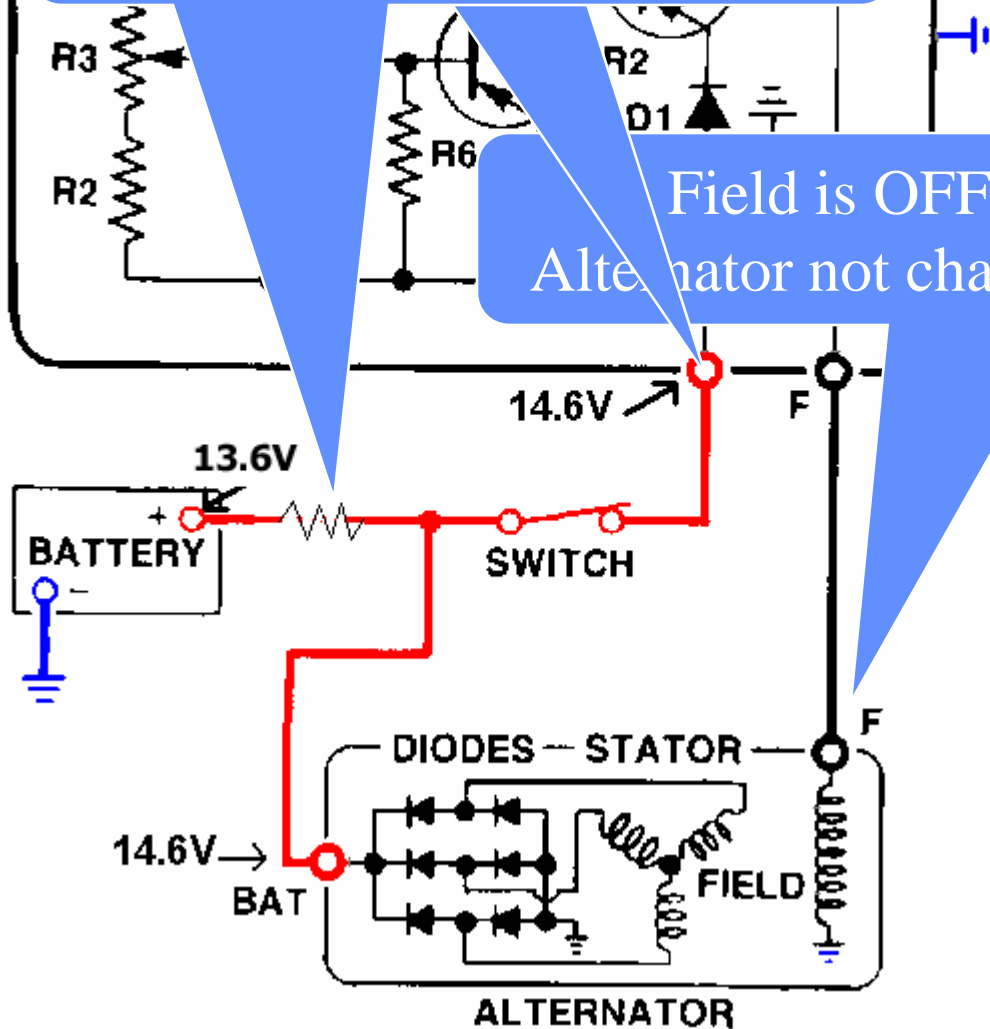

# Test the Charging System

- Test belts, battery condition and wiring to ensure trouble free power
- Test for Overcharging  
(with full charge on battery)
- Test for Undercharging
- Test for A/C voltage